

# DESIGN FOR TESTABILITY

GENERATING TESTS FOR LARGE CIRCUITS IS VERY TIME CONSUMING. ONE WAY TO GET AROUND THIS PROBLEM IS TO CONSTRAIN OR MODIFY THE DESIGN TO MAKE TEST GENERATION EASIER

MOST DFT TECHNIQUES ARE TARGETED TO SEQUENTIAL CIRCUITS WHERE TEST GENERATION IN GENERAL IS A DIFFICULT PROBLEM

IF TESTING IS NOT CONSIDERED DURING THE DESIGN PHASE VERY LOW FAULT COVERAGES CAN RESULT IN ADDITION TO HIGH TEST GENERATION TIMES  
⇒ DFT SAVES MONEY + TIME!

DFT TECHNIQUES CAN BE DIVIDED INTO:

- AD HOC TECHNIQUES
- STRUCTURED DESIGN TECHNIQUES
- SELF-TEST + BUILD-IN TESTING

THE OBJECTIVE OF DFT IS TO IMPROVE THE CONTROLLABILITY AND OBSERVABILITY OF INTERNAL CIRCUIT NODES SO THAT THE CIRCUIT CAN BE TESTED EFFECTIVELY:

### CONTROLLABILITY:

THE ABILITY TO SET OR RESET INTERNAL NODES FROM THE PRIMARY INPUTS

### OBSERVABILITY:


THE ABILITY TO OBSERVE THE VALUE OF AN INTERNAL NODE AT THE PRIMARY OUTPUTS

THESE ARE TWO GOOD MEASURES OF THE TESTABILITY OF A CIRCUIT, i.e. HOW EASY IT IS TO TEST. DESIGN FOR TESTABILITY ATTEMPTS TO IMPROVE CIRCUIT TESTABILITY BY MAKING THE INTERNAL NODES MORE CONTROLLABLE AND OBSERVABLE

# AD-HOC DFT TECHNIQUES


## (I) Test Points

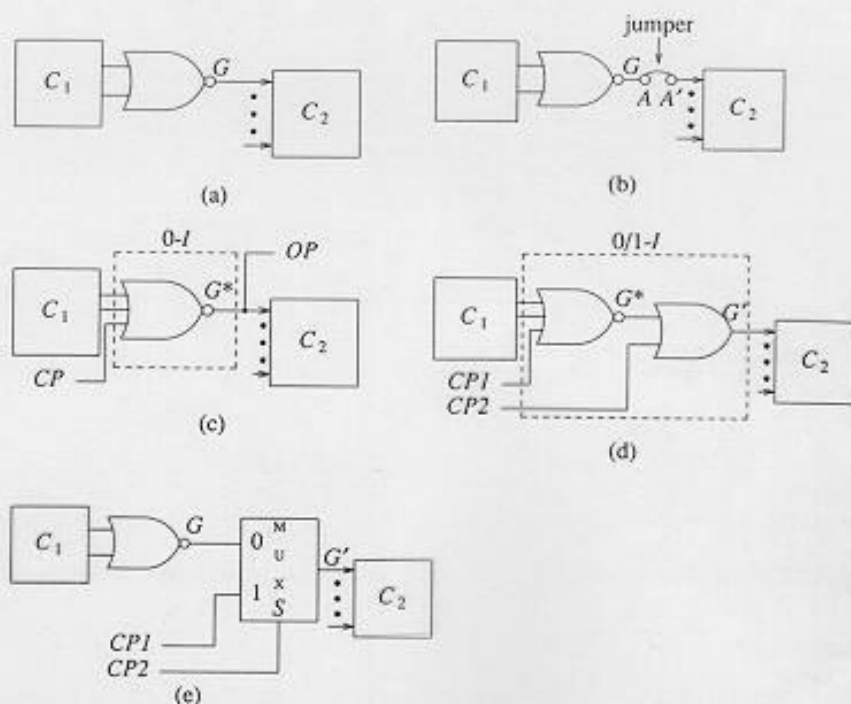- (a) ORIGINAL CIRCUIT
- (b) "JUMBER": EXTERNAL TEST EQUIPMENT CAN OBSERVE AND/OR INJECT LOGIC VALUES ON  $A/A'$ .
- (c)  $\phi$ -CONTROLLABILITY PLUS OBSERVABILITY
- (d)  $\phi$ -1-CONTROLLABILITY
- (e) 0-1-CONTROLLABILITY VIA THE USE OF A MULTIPLEXER




USING TEST POINTS REQUIRE A SIGNIFICANT NUMBER OF I/O PINS. TO ALLEVIATE THE PROBLEM WE USE THE FOLLOWING TRADE OFFS:


### MULTIPLEXING OBSERVATION POINTS

 

### CONTROLLABILITY VIA A DEMULTIPLEXER

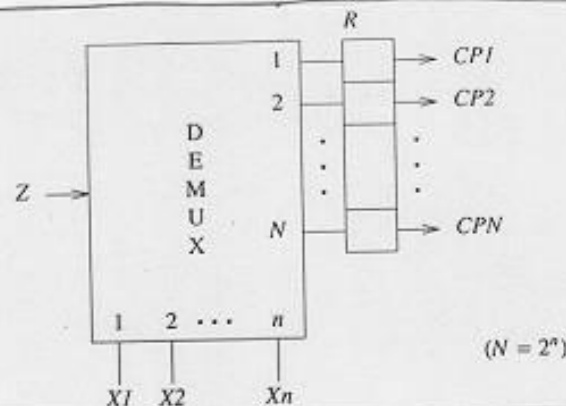


### TIME SHARING I/O PORTS

 


## (II) Initialization

DESIGN CIRCUITS SO THAT IT IS EASY TO INITIALIZE THEM
 
## (III) Counter and Shift Register Partitioning



(a)

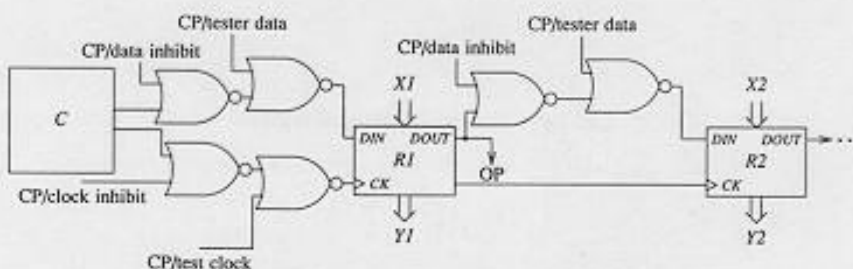

(b)

REGISTER  
 $R = R_1 + R_2$   
WITHOUT  
TESTABILITY  
FEATURE


... WITH  
TESTABILITY  
FEATURE

### SAVINGS:

16-bit counter needs  $2^{16} = 65536$  clock cycles.


"Partitioned" in 2 8-bit counters  
it needs  $2 \cdot 2^8 = 512$  clock cycles.
 
# (IV) Partitioning of large combinational structures



INSERT MULTIPLEXERS BETWEEN THE LARGE COMBINATIONAL STRUCTURE  $C = C_1 + C_2$ :

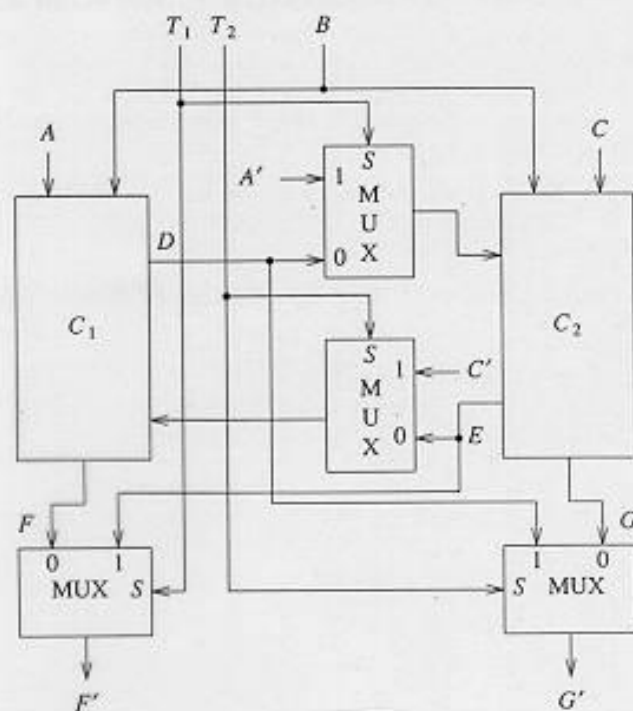- $T = 00$  normal operation
- $T = 01$  tests  $C_1$  as inputs to  $C_1$  are  $A$  and  $C'$  and it outputs to  $F$   $G'$
- $T = 10$  tests  $C_2$



$T_1$	$T_2$	Mode
0	0	normal
0	1	test $C_1$
1	0	test $C_2$

### Control points usually are:

- control, address, data buses
- enable/hold to microprocessors & memories
- data select to MUXes
- clock, presets to FFs, counters, shift registers

### Observation points usually are:

- stem lines with high Fanout
- redundant signal lines
- outputs of MUXes
- FFs, counters, shift registers
- address, control, data buses




# DFT WITH SCAN REGISTERS

TEST POINTS ARE EXPENSIVE IN TERMS OF I/O PINS.  
SCAN REGISTER (MADE WITH SCAN CELLS) IS  
A REGISTER WITH BOTH SHIFT AND PARALLEL-LOAD  
ABILITY. ITS SCAN CELLS CAN BE USED AS  
OBSERVATION AND/OR CONTROL POINTS.

TRADE OFF: Saves I/O pins increases test time  
and area overhead


## SCAN CELL

 


$\bar{N}/T = 0$  loads  
From D

$\bar{N}/T = 1$  loads  
From  $S_i$

## SCAN REGISTER

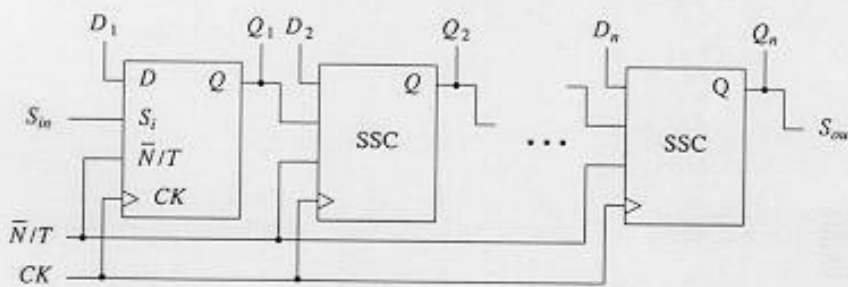

(c)

 

$\bar{N}/T = 1$  shifts  
From S


$\bar{N}/T = 0$  loads  
in parallel

SCAN IN: loading  
From  $S_{in}$


SCAN OUT: reading  
From  $S_{out}$



 
# Simultaneous Controllability and Observability



(a)

 

(b)

 


(c)


ORIGINAL  
CIRCUIT

TWO VARIANTS OF  
SIMULTANEOUS CONTROLLABILITY  
AND OBSERVABILITY (DEPENDING  
OF MUX'S SELECT LINE)


## NON-SIMULTANEOUS TECHNIQUES

 

(d)

 

(e)

 

(f)


OBSERVABILITY

OBSERVABILITY  
THROUGH  
COMPACTION

CONTROLLABILITY

# GENERIC SCAN-BASED DESIGNS

## FULL SERIAL INTEGRATED SCAN

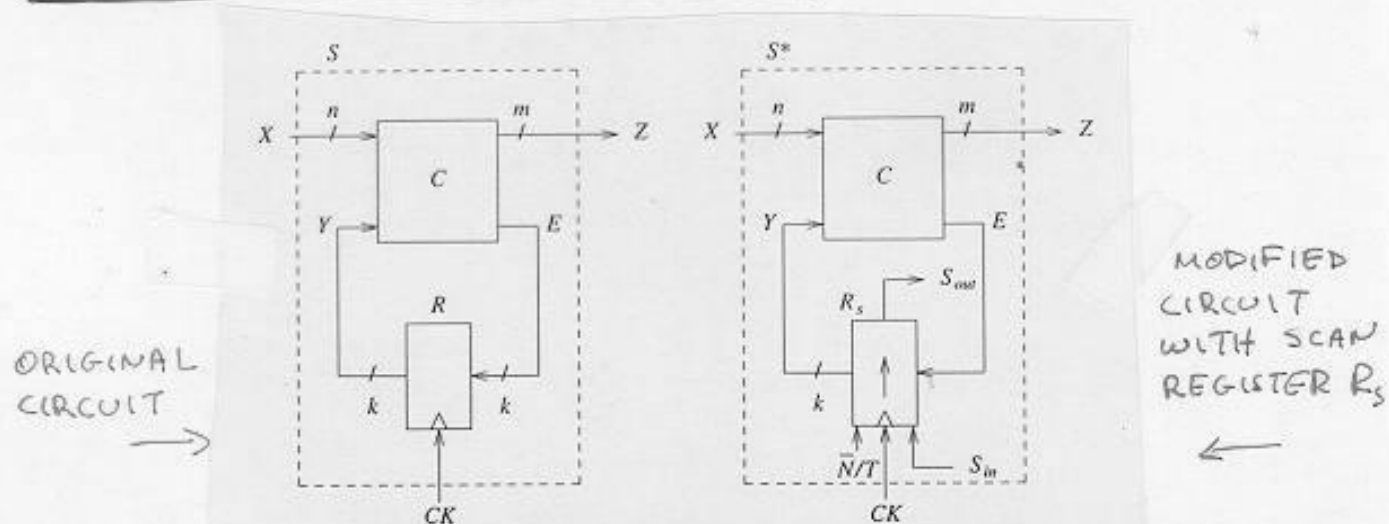

## TEST GENERATION + FAULT DETECTION ON MODIFIED CIRCUIT:

Run PODEM on combinational structure assuming  $Y$  and  $E$  are pseudo inputs/outputs.

You get a sequence of

$(x_1, y_1)$   $(x_2, y_2)$  ...

test vectors

$(z_1, e_1)$   $(z_2, e_2)$  ...

responses

To test the device:


Scan in  $y_1$  and at  $k^{\text{th}}$  clock cycle apply  $x_1$ .

After clock cycle load  $e_1$  in  $R_s$

and observe  $z_1$  etc...
 
## ISOLATED SERIAL SCAN


SCAN REGISTER IS NOT IN DATA PATH AS BEFORE  
(see Figure below)



IF  $|R_s| = |R|$  THEN WE HAVE FULL ISOLATED SCAN:

- accommodates on-line testing vs. Full serial
- hardware overhead


## NON-SERIAL SCAN

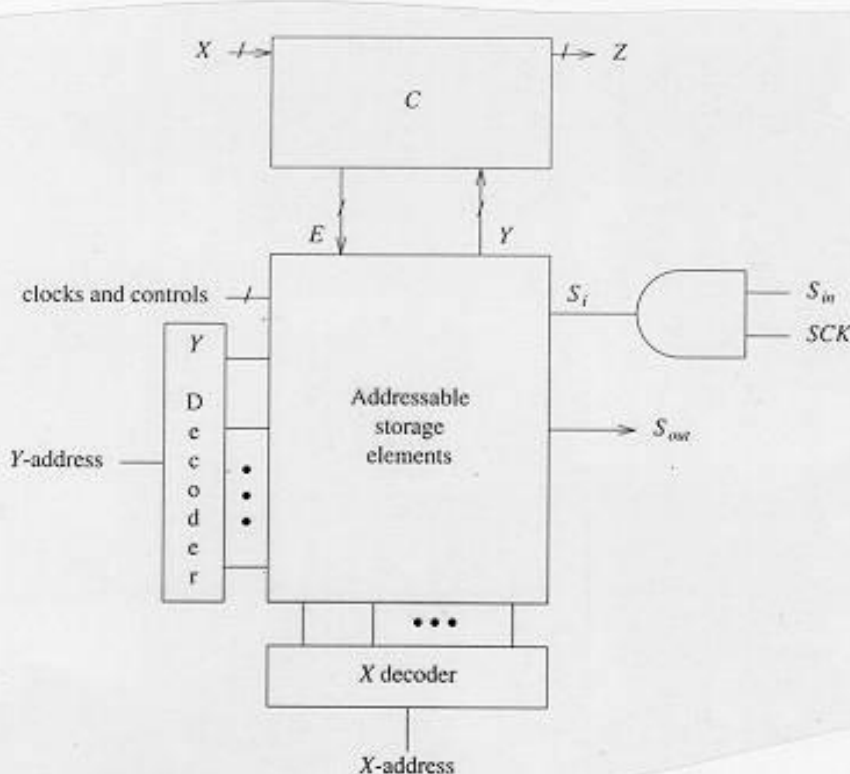


Improves  
scan-in/scan-out  
time but  
increases  
hardware  
overhead
 
# SCAN CELL DESIGNS

MOST OF THE TIMES IT IS USEFUL TO SEPARATE SYSTEM CLOCK FROM SCAN CLOCK:



 
TO AVOID PERFORMANCE DEGRADATION DUE TO MUX THE FOLLOWING 2-PORT SHIFT REGISTER LATCH WAS DESIGNED BY IBM:



NOTE: ONLY C-B OR A-B CLOCKS CAN BE ENABLED AT ANY TIME!
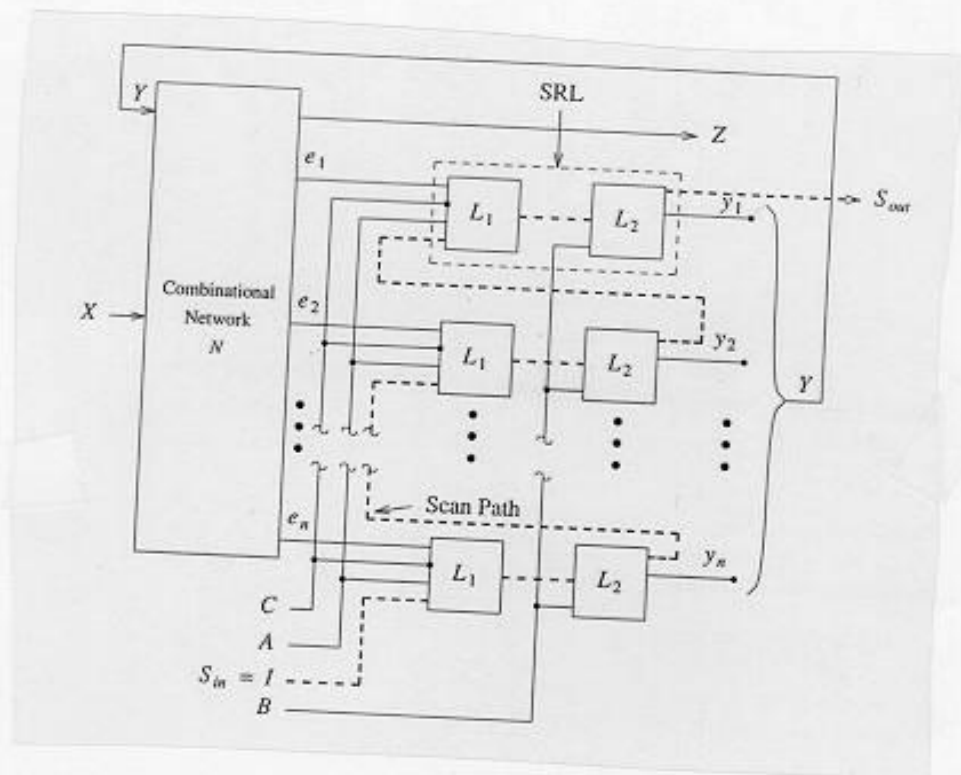
## Level Sensitive Scan Design

THE FOLLOWING DOUBLE-LATCH DESIGN USES THE DESIGN CELL DEVELOPED BY IBM AND SHOWN BEFORE.



THERE ARE OTHER LSSD SCHEMES WITH LESS GATES, MORE CLOCKING ETC. FINAL DECISION IS BASED UPON THE # OF ADDED COMBINATIONAL LOGIC TO THE CIRCUIT (TRADE-OFF)

## LSSD cont.

A SEQUENTIAL CIRCUIT IS LEVEL SENSITIVE IF ITS STEADY STATE RESPONSE TO ANY INPUT STATE CHANGE IS:

- independent of its inertial delays
- independent of the order which inputs change

IBM'S DISCIPLINE ACHIEVES THIS WITH LSSD.

DESIGN RULES:

- All internal latch storage must be implemented with hazard-free latches
- The two latches in the SLR must be controlled by two non-overlapping clocks
- All (respective) clocks for the same latch in the SLR must originate from same clock source


### ADVANTAGES:

Design is race free, hazard immune, and LSSD is not intrusive on design process


### DISADVANTAGES:

Latches are complex, overhead 4-20% in chip area, introduces 4 extra I/O pins and all timing is controlled by external clocks

# SYSTEM LEVEL TESTING

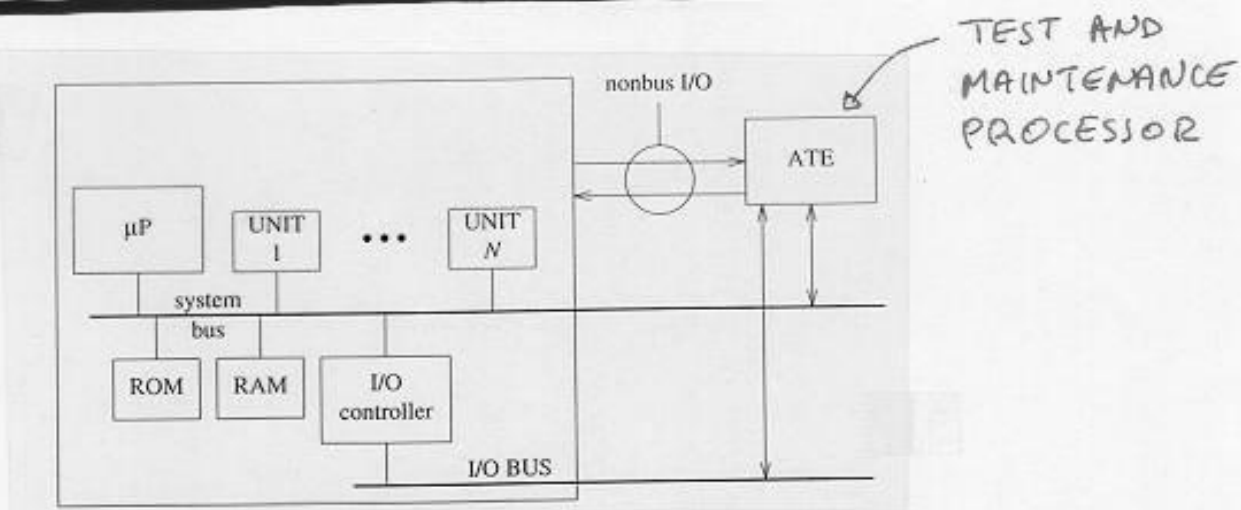


## A HIERARCHICAL DFT APPROACH

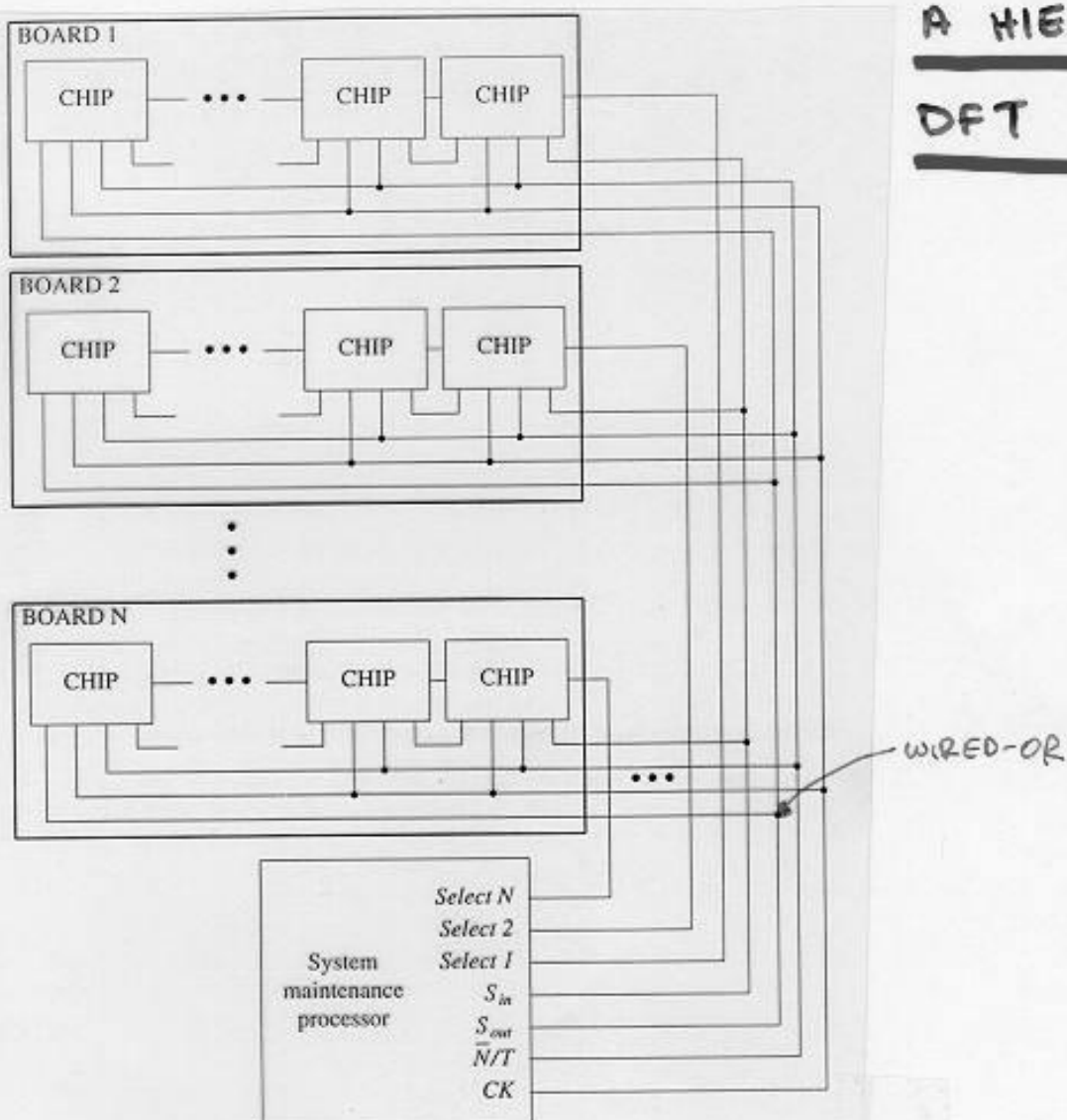



## MULTIPLE TEST SESSIONS

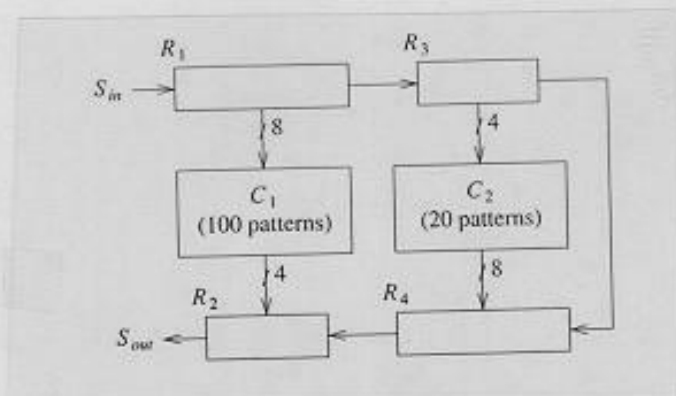


### TESTING IN OVERLAPPED MODE:

Test them as partly as one block of logic and partly as separate blocks.

- Test  $C_1$  and  $C_2$  with 20 patterns  
12 bits wide  $12 \times 20$  clock cycles
- Test  $C_1$  with remaining 80 patterns  
each 8 bits wide  $80 \times 8$  clock cycles

Total: 640 clock cycles

## MULTIPLE TEST SESSIONS

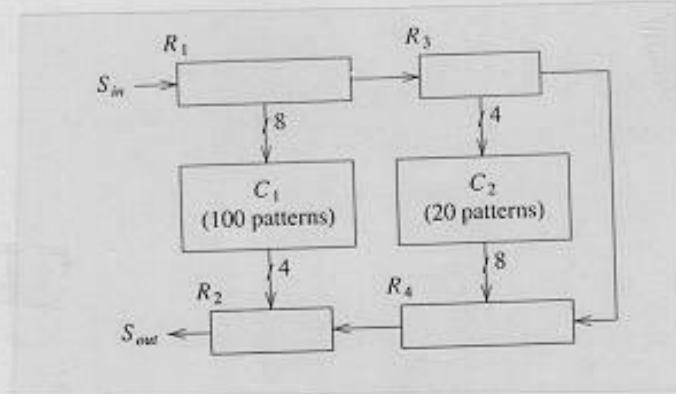

### TESTING IN "TOGETHER MODE":


$C_1$  requires 100 patterns

$C_2$  requires 20 patterns

Total:  $100 \times 12$  clock cycles

We ignore time to load  $R_2$  and  $R_4$  as well as scanning out Final result.

# MULTIPLE TEST SESSIONS

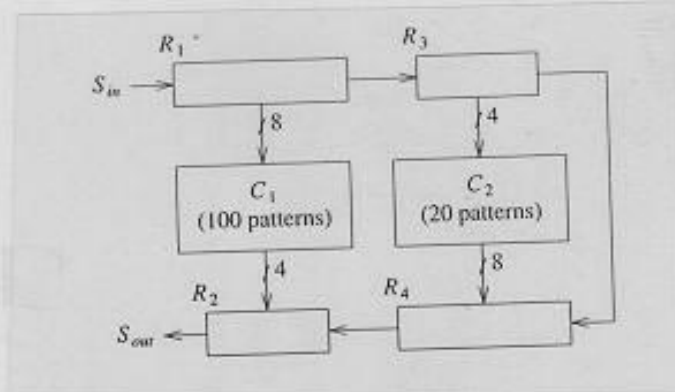

## TESTING IN "SEPARATE MODE":

While  $C_1$  is tested,  $C_2/R_3/R_4$  are ignored (and vice versa)

Testing  $C_1$  :  $8 \times 100$  clock cycles

Testing  $C_2$  :


redirect  $R_4$  to a PO and pad input test patterns with 4 don't cares

$8 \times 20$  clock cycles

Total: 960 clock cycles vs. 1200 before
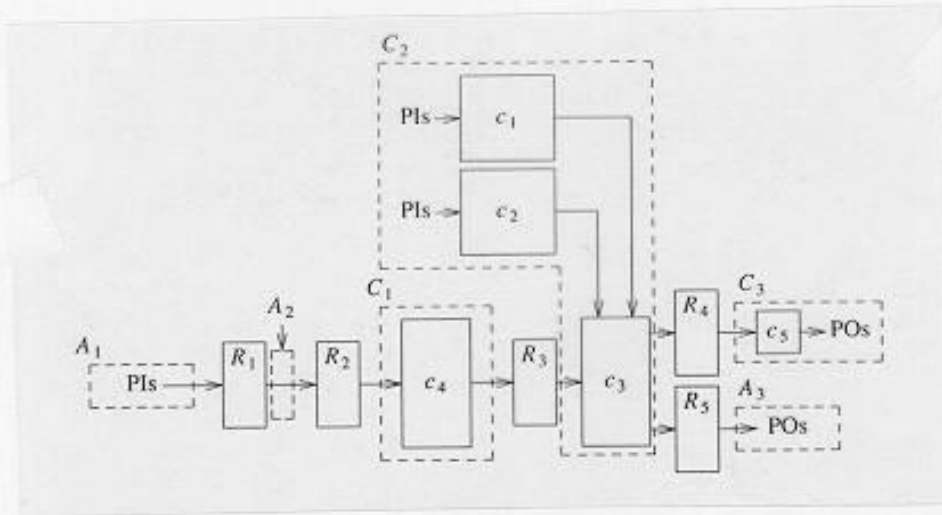
## CASE STUDY: BALLAST PARTIAL SCAN


CLOUD: A MAXIMAL REGION OF COMBINATIONAL (NON-EMPTY) LOGIC



BALANCED SEQUENTIAL CIRCUIT (or B-STRUCTURE):

WHEN FOR ANY TWO CLOUDS IN THE CIRCUIT ALL SIGNAL PATHS GO THROUGH THE SAME NUMBER OF REGISTERS.

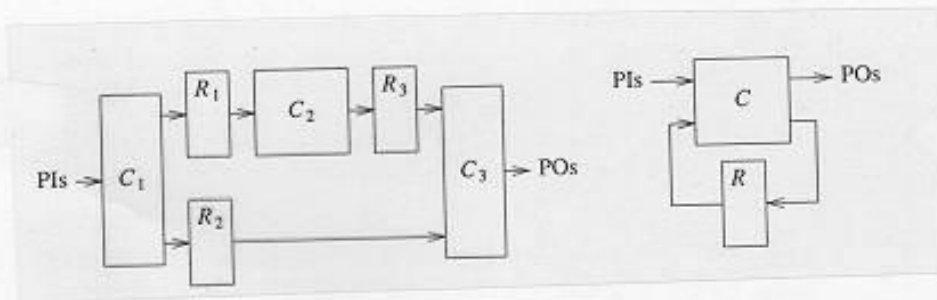$\Rightarrow$  Circuit above is B-STRUCTURE below they're not



### PROPOSITION

Any sequential circuit can be a B-STRUCTURE by replacing a set of appropriate registers into scan registers (NP-Complete problem)

### DEFINITIONS

- $C_B$  is the combinational equivalent of B-STRUCTURE  $S_B$  when FFs are replaced by wires
- Largest # of registers on any path  $S_B$  between two clouds is depth of  $S_B$

Let  $t_1, t_2, \dots, t_n$  vectors testing  $C_B$ , where (intuitively):  $t_i = \underbrace{t_i^{PI}}_{\rightarrow PIS} + \underbrace{t_i^{PPI}}_{\rightarrow \text{scan inputs}}$

### ALGORITHM: Testing $S_B$ (depth $d$ )

Scan  $t_i^{PPI}$  and apply  $t_i^{PI}$


Hold values above and clock circuit  $d$  times

Place scan path in normal mode and clock it once

observe POs

REPEAT w/ NEXT VECTOR

Ex:

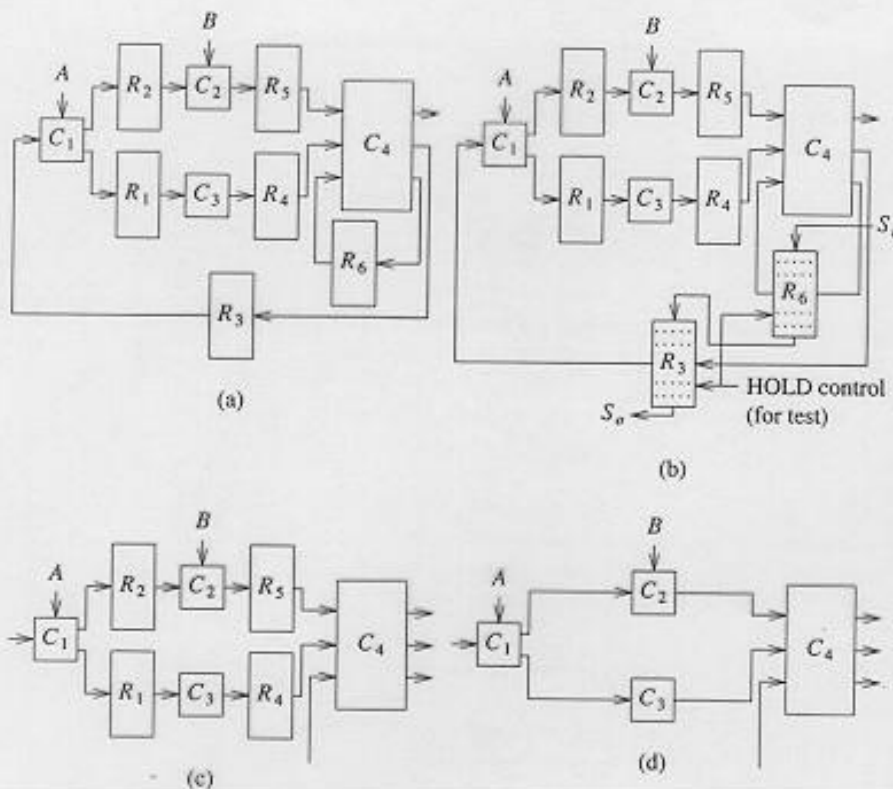

(a) original circuit

(b) R<sub>3</sub>/R<sub>6</sub> selected as scan registers

(c) replacing scan registers with PIs/POs

(d) CB (depth = 2)

clock cycle 1: results at R<sub>1</sub>/R<sub>2</sub>

clock cycle 2: results at R<sub>5</sub>/R<sub>4</sub>

clock cycle 3: results at POs