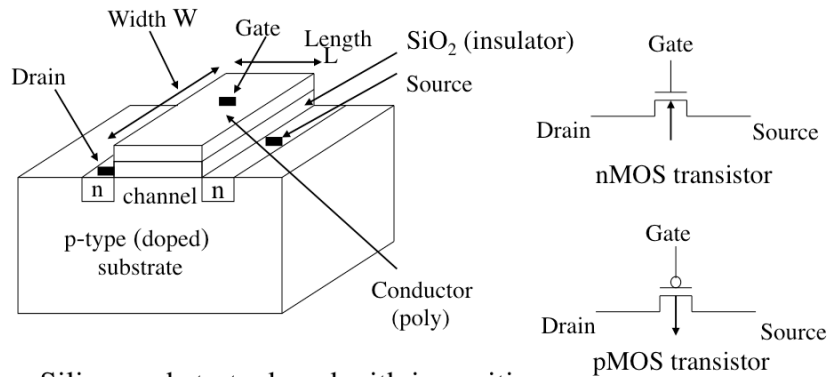



# MOS Transistors



- Silicon substrate doped with impurities
- Adding or cutting away insulating glass ( $\text{SiO}_2$ )
- Adding wires made of polycrystalline silicon (*polysilicon*, *poly*) or metal, insulated from the substrate by  $\text{SiO}_2$


1

# MOS Transistor Switches

 

2

## MOS Transistor Switches

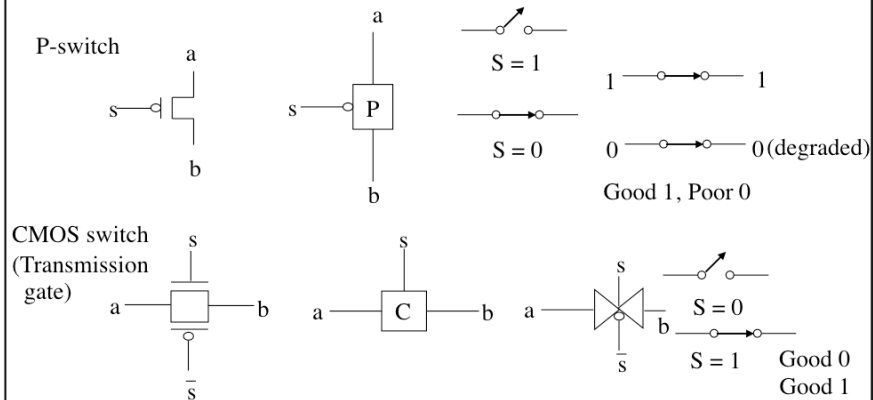

3


## Signal Strength

- *Strength* of signal
  - How close it approximates ideal voltage source
- $V_{DD}$  and GND rails are strongest 1 and 0
- nMOS pass strong 0
  - But degraded or weak 1
- pMOS pass strong 1
  - But degraded or weak 0
- Thus nMOS are best for pull-down network

4

## Pass Transistors


- Transistors can be used as switches

 

5
 
## Transmission Gates


- Pass transistors produce degraded outputs
- Transmission gates* pass both 0 and 1 well



6
 
# Complementary CMOS

- Complementary CMOS logic gates
  - nMOS *pull-down network*
  - pMOS *pull-up network*
  - a.k.a. static CMOS




	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (not allowed)

7
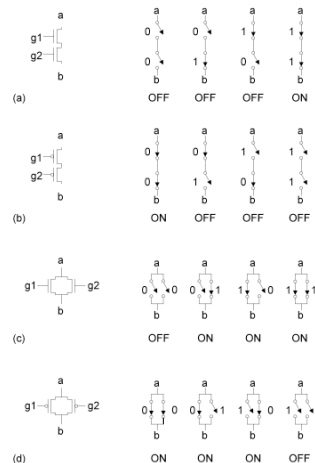
# Series and Parallel


- nMOS: 1 = ON
- pMOS: 0 = ON
- Series*: both must be ON
- Parallel*: either can be ON





8
 
## Conduction Complement

- Complementary CMOS gates always produce 0 or 1
- Ex: NAND gate
  - Series nMOS:  $Y=0$  when both inputs are 1
  - Thus  $Y=1$  when either input is 0
  - Requires parallel pMOS
- Rule of *Conduction Complements*
  - Pull-up network is complement of pull-down
  - Parallel  $\rightarrow$  series, series  $\rightarrow$  parallel



## CMOS Logic Gates-1

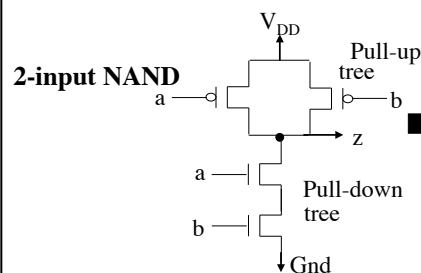 

Pull-down truth table

a	b	z
0	0	Z
0	1	Z
1	0	Z
1	1	0

Pull-up truth table


a	b	z
0	0	1
0	1	1
1	0	1
1	1	Z

NAND truth table

a	b	z
0	0	1
0	1	1
1	0	1
1	1	0

## CMOS Logic Gates-2

### 2-input NOR

 

Pull-down truth table		
a	b	z
0	0	Z
0	1	0
1	0	0
1	1	0


Pull-up truth table		
a	b	z
0	0	1
0	1	Z
1	0	Z
1	1	Z

NOR truth table		
a	b	z
0	0	1
0	1	0
1	0	0
1	1	0

- There is always (for all input combinations) a path from *either* 1 or 0 to the output
- No direct path from 1 to 0 (low power dissipation)
- *Fully restored* logic
- No ratio-ing is necessary (*ratio-less* logic)
- Generalize to n-input NAND and n-input NOR?

11

## CMOS Compound (Complex) Gates-1

 


- What function is implemented by this circuit?

12

## Compound Gates-2

How to implement  
 $F = ab + bc + ca$ ?

•  $F = ab + bc + ca$

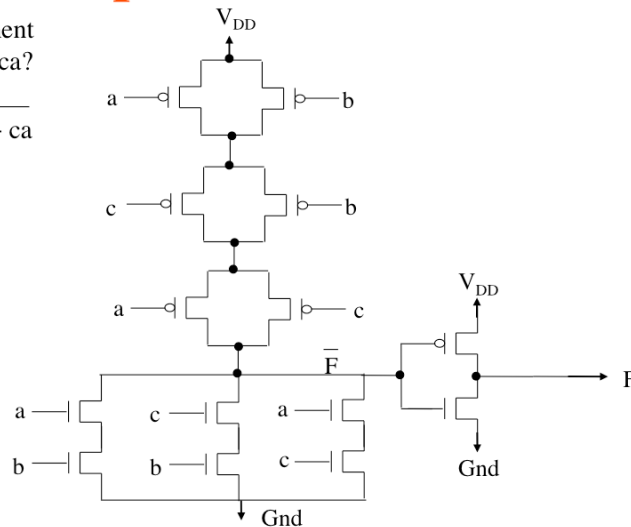


13

## Compound Gates

- *Compound gates* can do any inverting function

- Ex:

 
$Y = \overline{A \cdot B + C \cdot D}$  (AND-AND-OR-INVERT, AOI22)



14

## Example: O3AI

$$Y = \overline{(A + B + C) \cdot D}$$

 


15

## CMOS Multiplexers

- Transmission gate implementation ( 4 transistors)

- Assume  $\bar{s}$  is available

 


- Complex gate implementation based on  $\bar{F} = \overline{as + b\bar{s}}$  requires 10 transistors

16




## And-Or-Invert (AOI) Gates

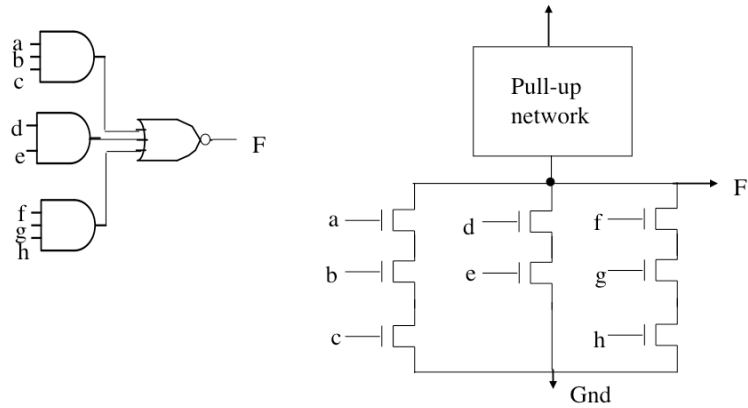

17

## Or-And-Invert (OAI) Gate

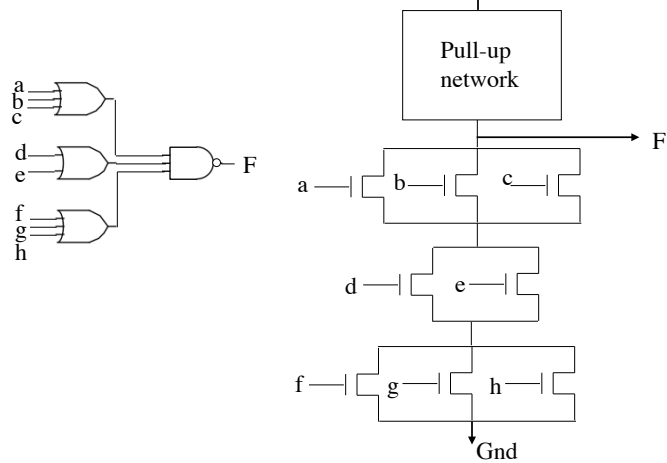

- Generally, complex CMOS gates can be derived directly from maxterms of the function (as in a Karnaugh map)

18


## Designing Complex Gates Using K-Maps

		cd			
		00	01	11	10
ab	00	1	1	1	1
	01	1	0	0	0
	11	0	0	0	0
	10	1	1	1	1

$$\bar{F} = ab + bd + bc$$

$$= b(a+d+c)$$
 
$$F = \bar{b} + \bar{a}\bar{c}\bar{d} \quad (\text{how many transistors?})$$



19


## Graph Models

How to generate pull-up circuit from the pull-down circuit?

- Draw pull-down graph for pull-down circuit
  - Every vertex is a source-drain connection
  - Every edge is an nMOS transistor
- Generate pull-up graph from the pull-down graph
  - Add vertex for every “region” of pull-down graph
  - Add edge between vertices lying in adjacent “regions”
  - Pull-up circuit corresponds to pull-up graph

20

## Graph Models

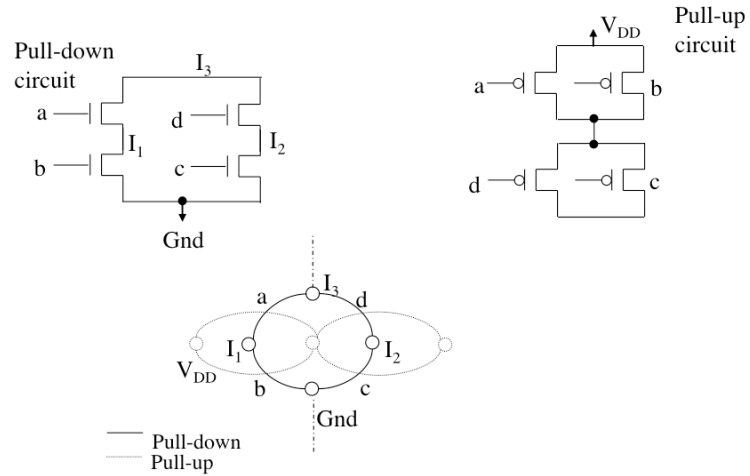


21

## Tristates

- *Tristate buffer* produces Z when not enabled


EN	A	Y
0	0	
0	1	
1	0	
1	1	

 

22
 
## Nonrestoring Tristate


- Transmission gate acts as tristate buffer
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y



23
 
## Tristate Inverter

- Tristate inverter produces restored output
  - Violates conduction complement rule
  - Because we want a Z output




24

# Multiplexers

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	


 


25

## Gate-Level Mux Design

$$Y = SD_1 + \bar{S}D_0 \text{ (too many transistors)}$$


- How many transistors are needed? 20

  

26
 
## Transmission Gate Mux


- Nonrestoring mux uses two transmission gates
  - Only 4 transistors



27
 
## Inverting Mux


- Inverting multiplexer
  - Use compound AOI22
  - Or pair of tristate inverters
  - Essentially the same thing
- Noninverting multiplexer adds an inverter



28

## CMOS Exclusive-Nor Gate

- 8-transistor implementation

 



a	b	TG <sub>1</sub>	TG <sub>2</sub>	F
0	0	nonconducting	conducting	$\overline{B}$ (1)
0	1	nonconducting	conducting	$\overline{B}$ (0)
1	0	conducting	nonconducting	$\overline{B}$ (0)
1	1	conducting	nonconducting	$\overline{B}$ (1)

- Better, 6-transistor implementation is possible!

29

## 4:1 Multiplexer

  
- 4:1 mux chooses one of 4 inputs using two selects
  - Two levels of 2:1 muxes
  - Or four tristates



30
 
## D Latch


- When CLK = 1, latch is *transparent*
  - D flows through to Q like a buffer
- When CLK = 0, the latch is *opaque*
  - Q holds its old value independent of D
- a.k.a. *transparent latch* or *level-sensitive latch*



31
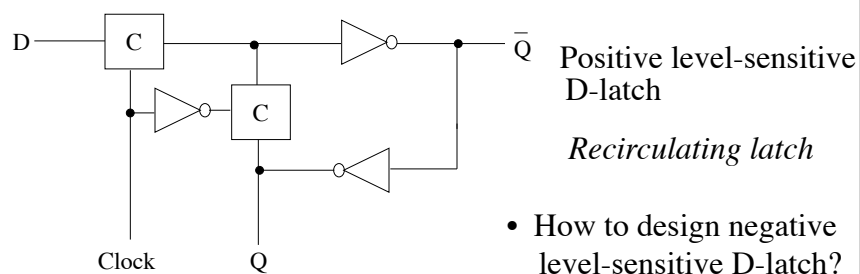
## Memory Elements: Latches and Flip-Flops

- Difference between a latch and a flip-flop?




- How to design negative level-sensitive D-latch?

32




## D Latch Design

- Multiplexer chooses D or old Q

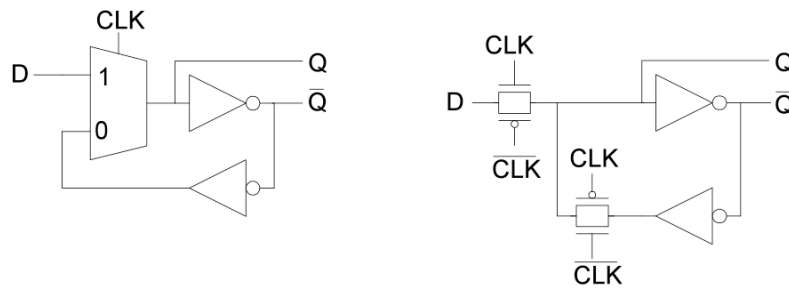


33
 
## Memory Elements: Latches and Flip-Flops



34


## D Latch Operation

 

35
 
## D Flip-flop


- When  $CLK$  rises,  $D$  is copied to  $Q$
- At all other times,  $Q$  holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*



36


## D Flip-flop Design

- Built from master and slave D latches

 


37

## Flip-Flop Design

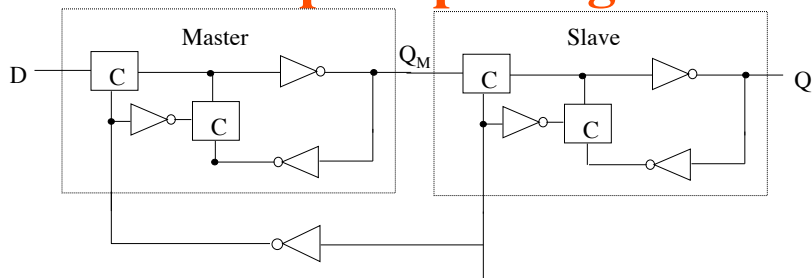


 - Positive edge-triggered D flip-flop
- How do we obtain the  $\bar{Q}$  output?



38


## D Flip-flop Operation

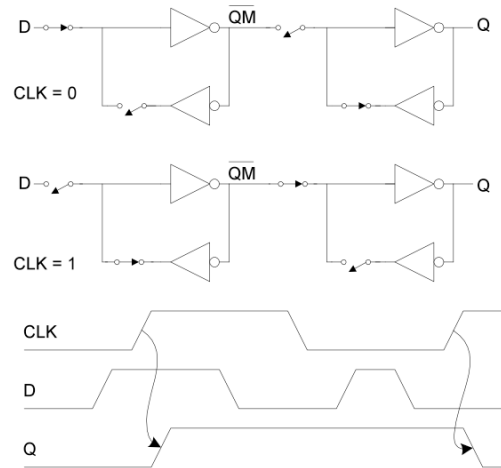

39
 
## Race Condition


- Back-to-back flops can malfunction from clock skew
  - Second flip-flop fires late
  - Sees first flip-flop change and captures its result
  - Called *hold-time failure* or *race condition*



40
 
## Nonoverlapping Clocks

- Nonoverlapping clocks can prevent races
  - As long as nonoverlap exceeds clock skew
- We will use them in this class for safe design
  - Industry manages skew more carefully instead




41
 
## Design Representation Levels

- Design domains
  - Behavioral
  - Structural
  - Physical

Gajski and Kuhn's Y-chart  
(layered like an onion)



- Hardware description languages commonly used at behavioral level, e.g. VHDL, Verilog
- Example: Consider the carry function  $c_o = ab + bc + c_i a$

42

## Verilog Example (Behavioral)

Boolean equation form:

```
module carry (co, a, b, ci);
output co;
input a, b, ci;
assign
    co = (a & b) | (a & ci) | (b & ci);
end module
```

Timing information:

```
module carry (co, a, b, ci);
output co;
input a, b, ci;
Wire #10 co = (a & b) | (a & ci) | (b & ci);
end module
```

c<sub>o</sub> changes 10 time units after a, b, or c changes

Boolean truth table form:

```
primitive carry (co, a, b, ci);
output co;
input a, b, ci;
table
    // a b c co
    1 1 ? : 1;
    1 ? 1 : 1;
    ? 1 1 : 1;
    0 0 ? : 0;
    0 ? 0 : 0;
    ? 0 0 : 0;
end table
end module
```

43

## Verilog Example (Structural)

Structural representation of 4-bit adder (top-down) :

```
module add4 (s, c4, ci, a, b);
output [3:0] s;
output [3:0] c4;
input [3:0] a, b;
input ci;
wire [2:0] co;
    add a0 (co[0], s[0], a[0], b[0], ci);
    add a1 (co[1], ..., b[1], co[0]);
    add a2 (co[2], ..., co[1]);
    add a3 (c4, s[3], a[3], b[3], co[2]);
end module
```

3-bit  
internal  
signal  
⇒

```
module add (co, s, a, b, ci);
output s, co;
input a, b, ci;
sum s1 (s, a, b, ci);
carry c1 (co, a, b, ci);
end module
```

↓

```
module carry (co, a, b, ci);
output co;
input a, b, ci;
wire x, y, z;
and g1 (y, z, b);
and g2 (z, b, ci);
and g3 (z, a, ci);
or g4 (co, x, y, z);
end module
```

*Technology-independent*

44