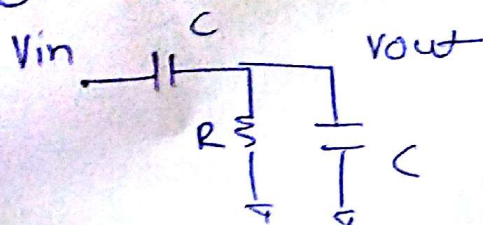



megachips test

①




Plot Response

②

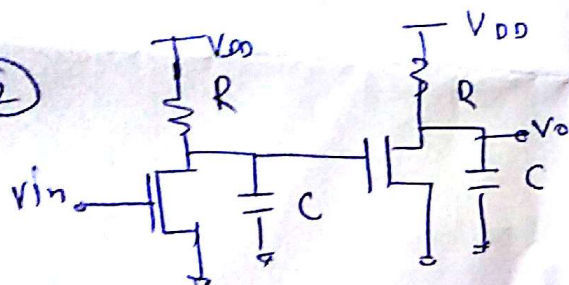


Plot V_o/V_{in}

③

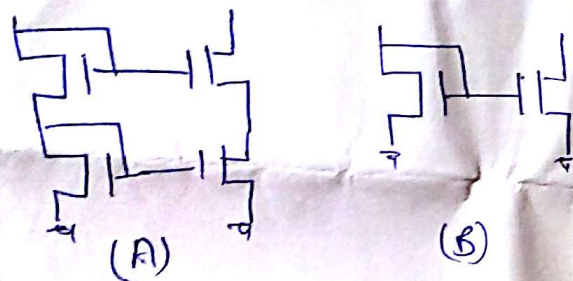


which is better and why

④

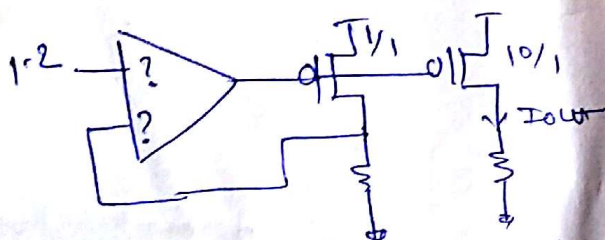

find Polarity for stability and

⑤

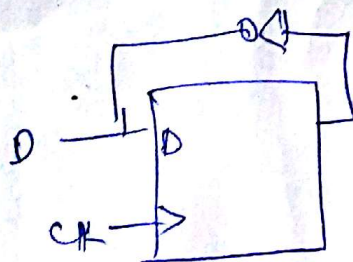


Find f_{max} ?

$t_{CLK-Q} = 50p$

$t_{inv} = 10p$

$t_{set} = 50p$ $t_{hold} = 50p$

⑥

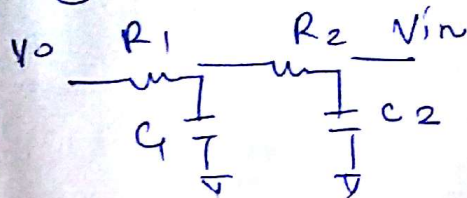


~~find~~ estimate delay

⑦ stability margins

$$H(s) = \frac{100(s+10)}{(s+0.001)(s+1000)}$$

⑧

interview

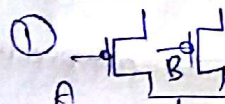

how do you order them for min delay

② why cascode is better than single stage (5 reasons)

③ static comparators

④ folded cascode

⑤ differential amp

⑥ diff amp vs two CS amp

⑦ dynamic latch comp design & constraints

⑧ interster of amplifier


⑨ Small signal model of inverter.

OH Semi
interview

① ADC explain \rightarrow (1 hour)

They asked everything about this


②

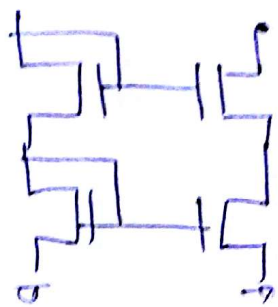

$V_{min} = ?$

V_{min} to operate this current mirror
benefits of using this over simple one




③ draw folded cascode op-amp so I drew

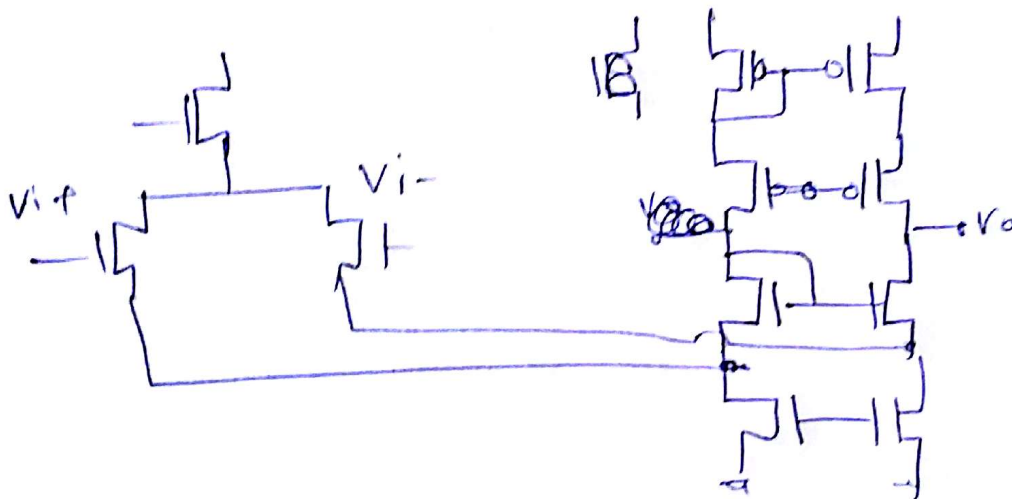

he asked me how will modify the PM and SR.

④ o/p char of MOS and explain. (20)

⑤ inverter as an amplifier

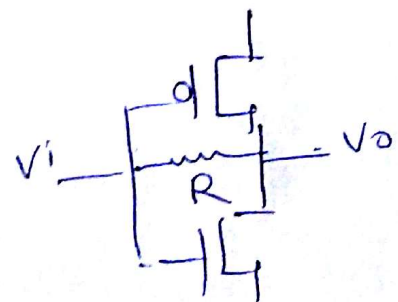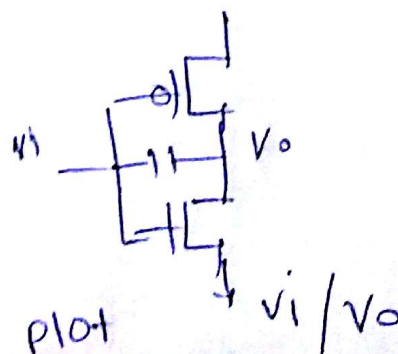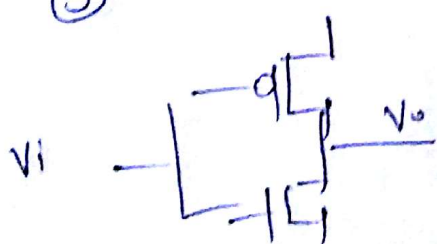


Texas instruments



written test

① pm and gm
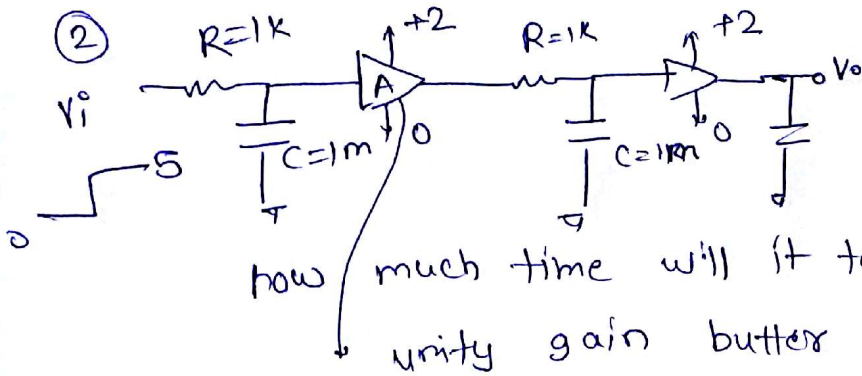
$$H(s) = \frac{100(s+10)}{(s+0.001)(s+1000)}$$



③

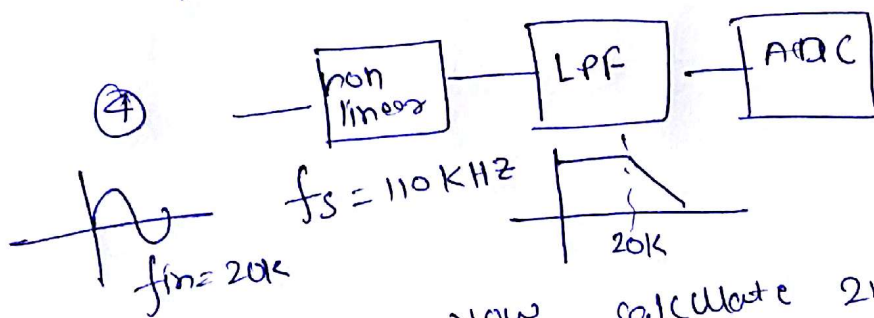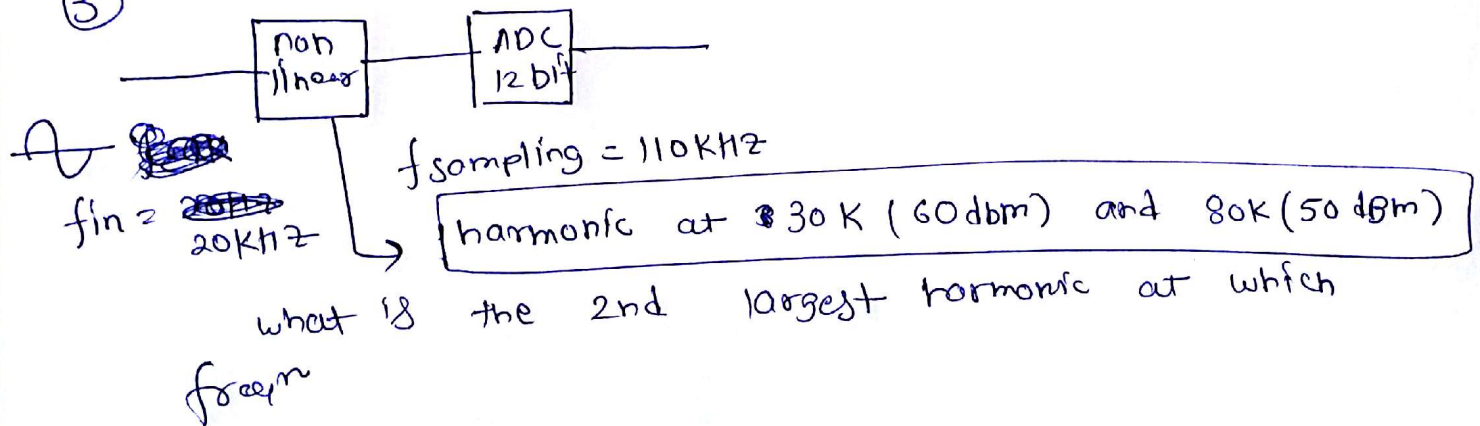

now calculate 2nd largest harmonic.






⑤ i don't remember other questions but they were difficult like above

aptitude was also time consuming (20 question)


20+20 = 40 in (75 min) So prepare hard for it.

TI interview

1st round

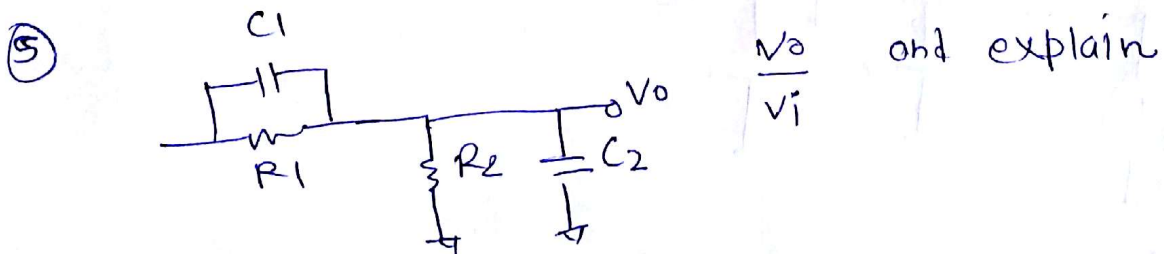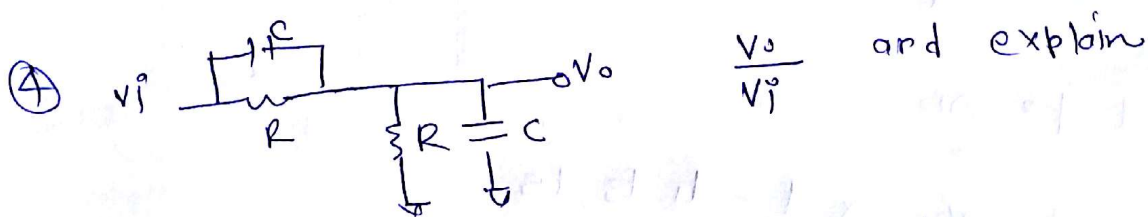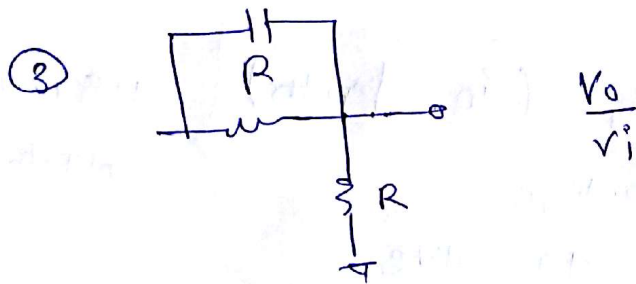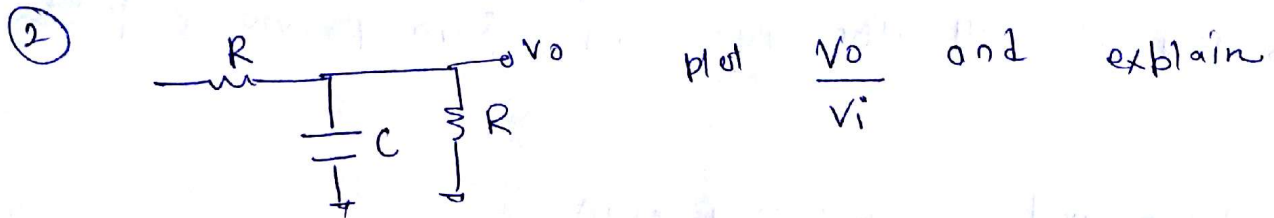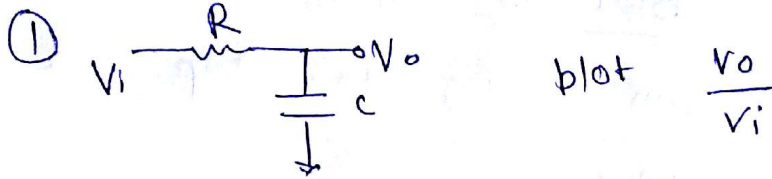


⑥ what is an integrator

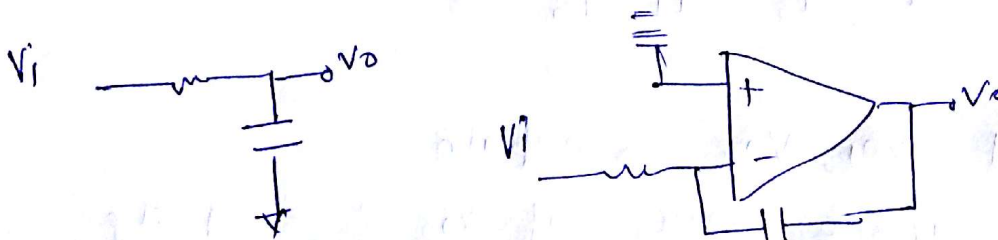

How they are different?

will they work for every kind of signal?
↓
(integrate)

TI interview

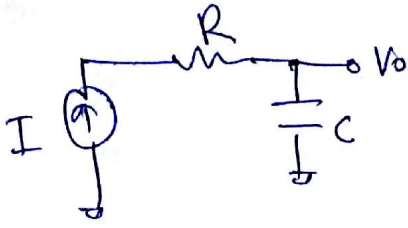

plot V_o and where it
will going to stop and



why.

⇒ Repeat all the questions from previous page

2nd round → 1st person


- About thesis
 - ~~plot~~ bottom plate sampling (in depth)
 - advantage & disadvantage
 - Some ^{mult} Capacitor circuit to solve
- 1.5 hours
(only thesis)

2nd person

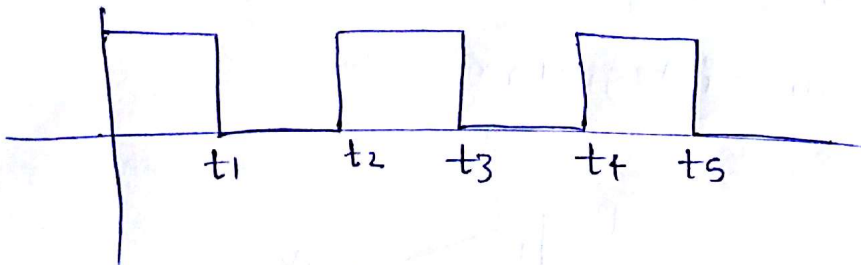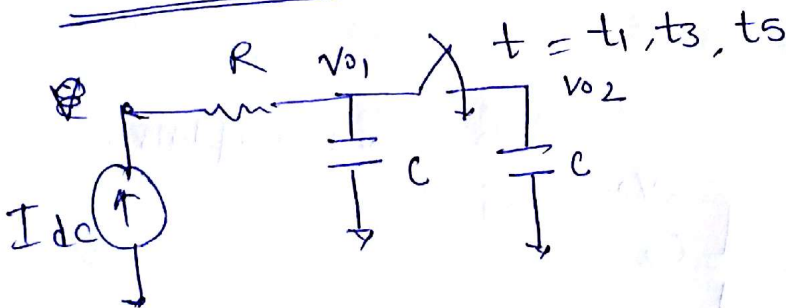


plot V_{o1} , V_{o2} → explain
average value of V_{o2} ? and its signi-
ficance.

TI Interview

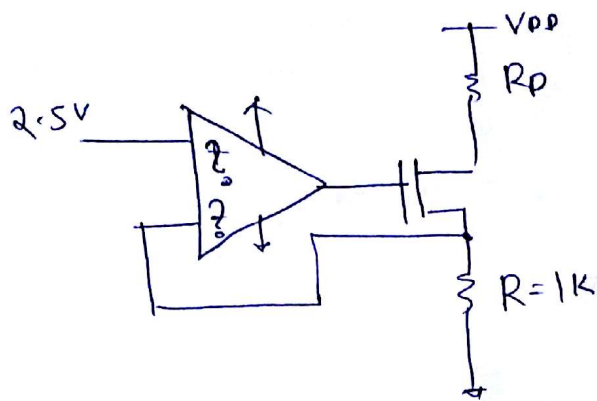


determine polarity for
stable system and
explain

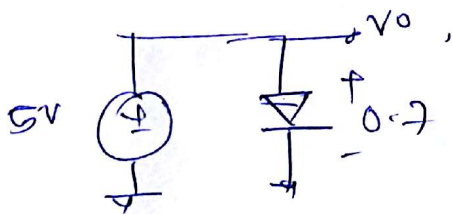-
- What is op-amp
 - explain virtual short concept at transistor level as well as block level
 - From ~~previous~~ previous questions they asked lot of questions.
-



$V_o = ?$

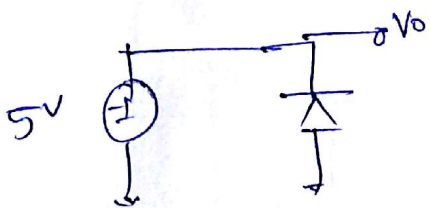

$V_o = ?$

