



Half Adder, Full Adder, Ripple Carry adder


Silicon Community - Varun Kouda

Half Adder - Truth table



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Adder - Boolean expression



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \overline{A}B + A\overline{B} = A \oplus B$$

$$C = AB$$

Half Adder - Digital Circuit Diagram


$$S = \overline{A}B + A\overline{B} = A \oplus B$$

$$C = AB$$

Logic Circuit



Full Adder - Truth Table


 


A	B	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder - Boolean expression

$$S = A \oplus B \oplus C_{in}$$

  
$$C_{out} = AB + BC_{in} + AC_{in} = AB + C_{in}(A \oplus B)$$



Full Adder - Digital Circuit diagram

$$S = A \oplus B \oplus C_{in}$$

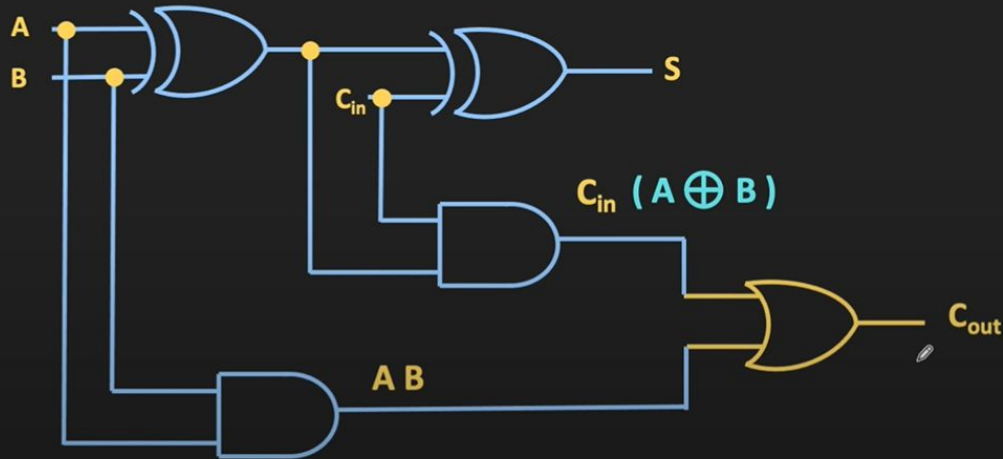
$$C_{out} = AB + BC_{in} + AC_{in} = AB + C_{in} (A \oplus B)$$




Full Adder using Half Adder

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + C_{in} (A \oplus B)$$

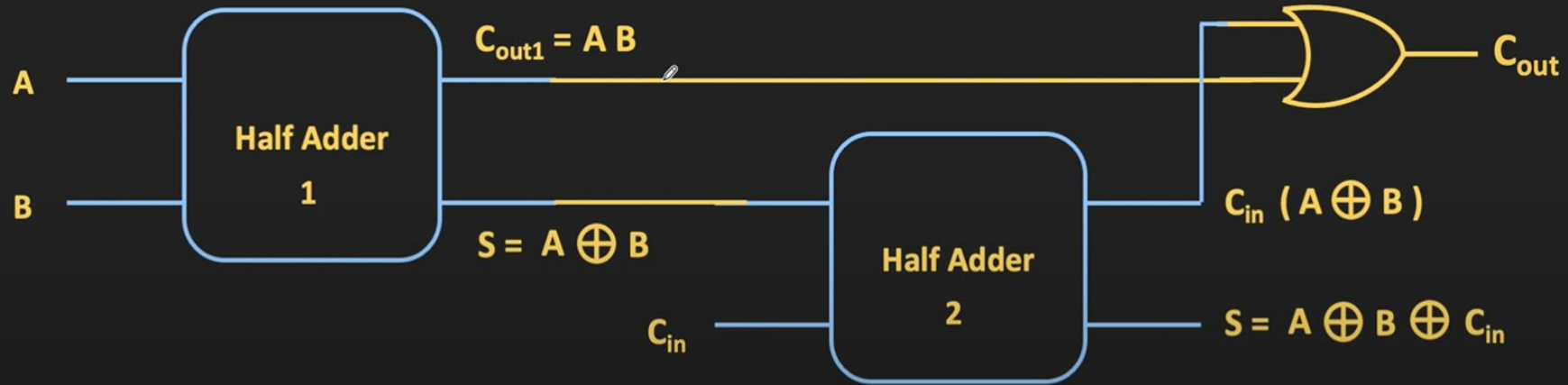

Ripple Carry Adder (4 - bit)

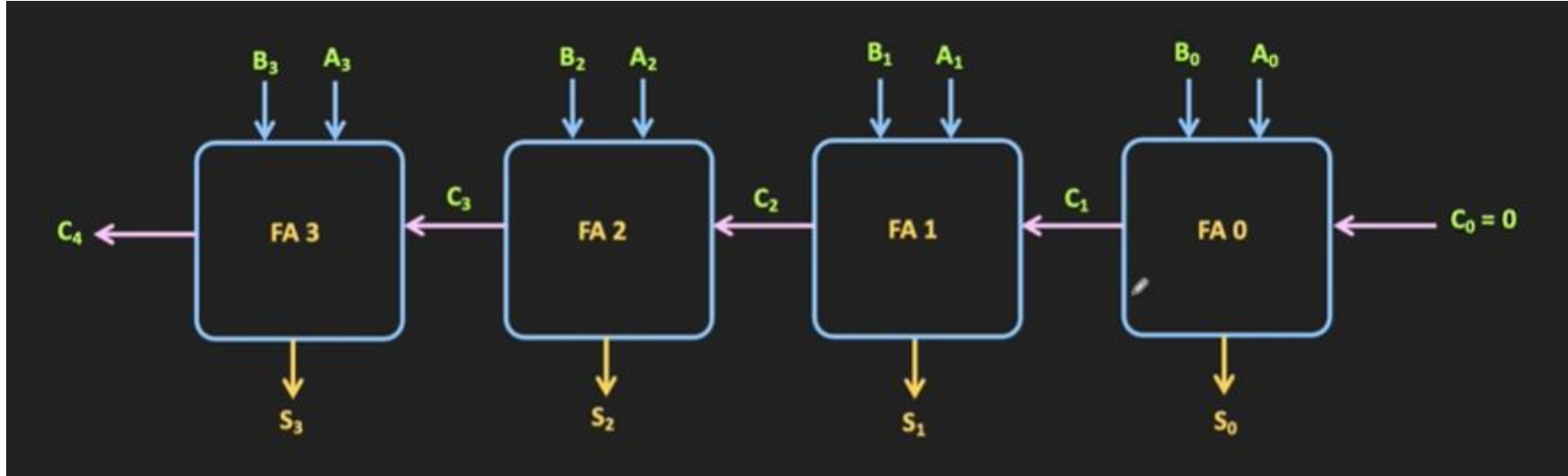


S₀, S₁, S₂ and S₃ are the Sums of 4 bit adder
C₁, C₂, C₃ and C₄ are carry forwards of 4 bit adder

Ripple Carry Adder - disadvantage

Let us suppose propagation delay for sum is $T(s)$

And propagation delay of Carry is $T(c)$

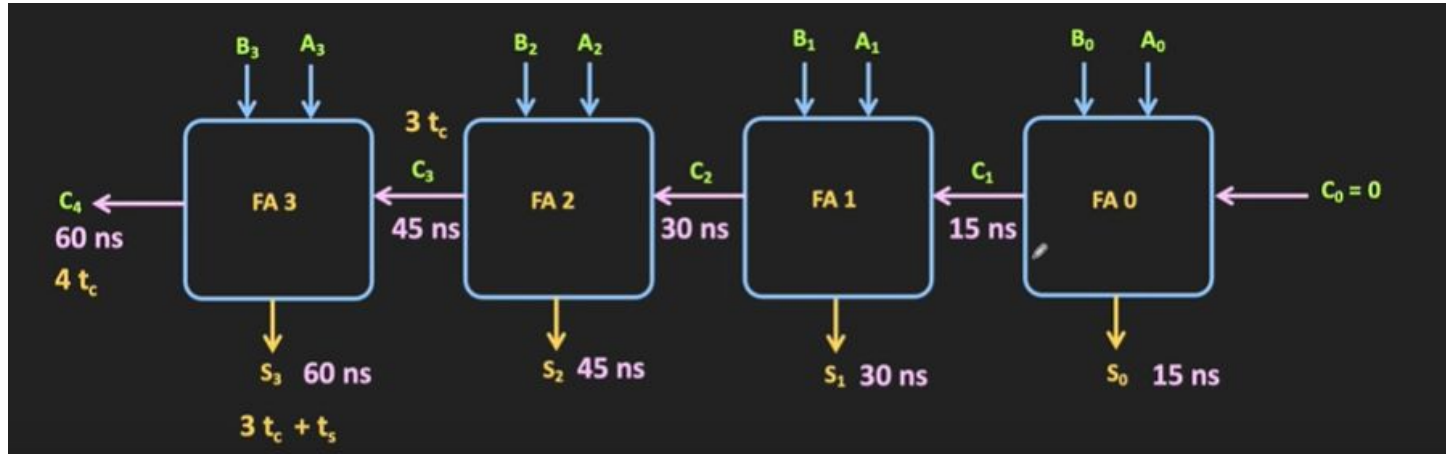Let $T(s) = 15\text{ns}$ and $T(c) = 15\text{ns}$



Ripple Carry Adder - Disadvantage



For 4 bit adder

Delay for sum = $3T(s) + 4T(c)$

Delay for carry = $4T(c)$

For n bit adder

Delay for sum = $(n-1)T(s) + nT(c)$

Delay for carry = $nT(c)$

So, ripple carry adder has this delay for giving the results out


Ripple Carry Adder - Example




In the Previous slide, we have seen total propagation delay for sum and carry of ripple carry adder when given propagation delay of sum and carry of each full adder

Now, here we will see the propagation delay for sum and carry of n bit ripple carry adder if propagation delay of XOR gate is $T(xor)$ and propagation delay of AND and OR gate is $T(p)$

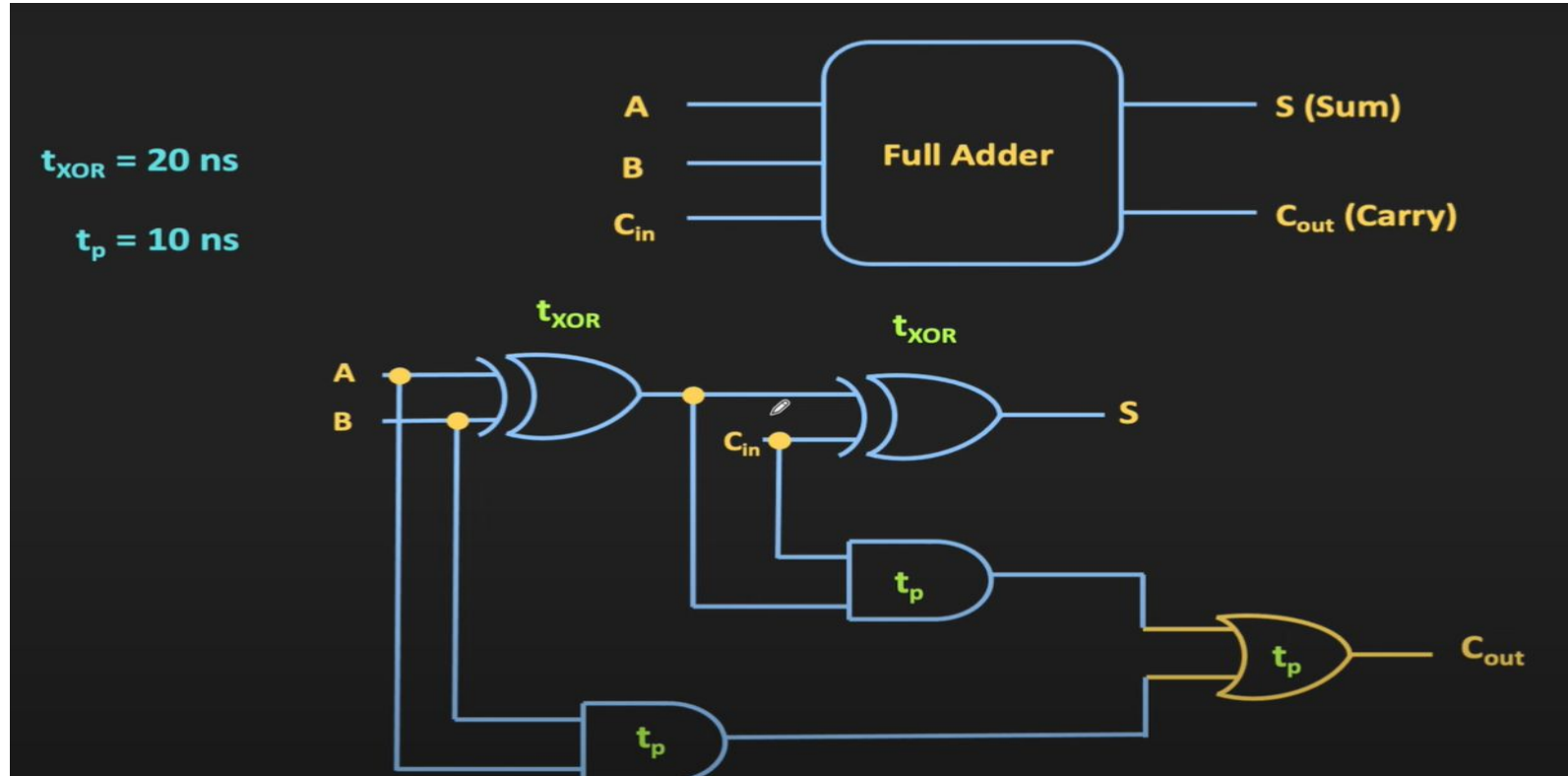Prop delay of Ripple Carry Adder with gate delays (1)



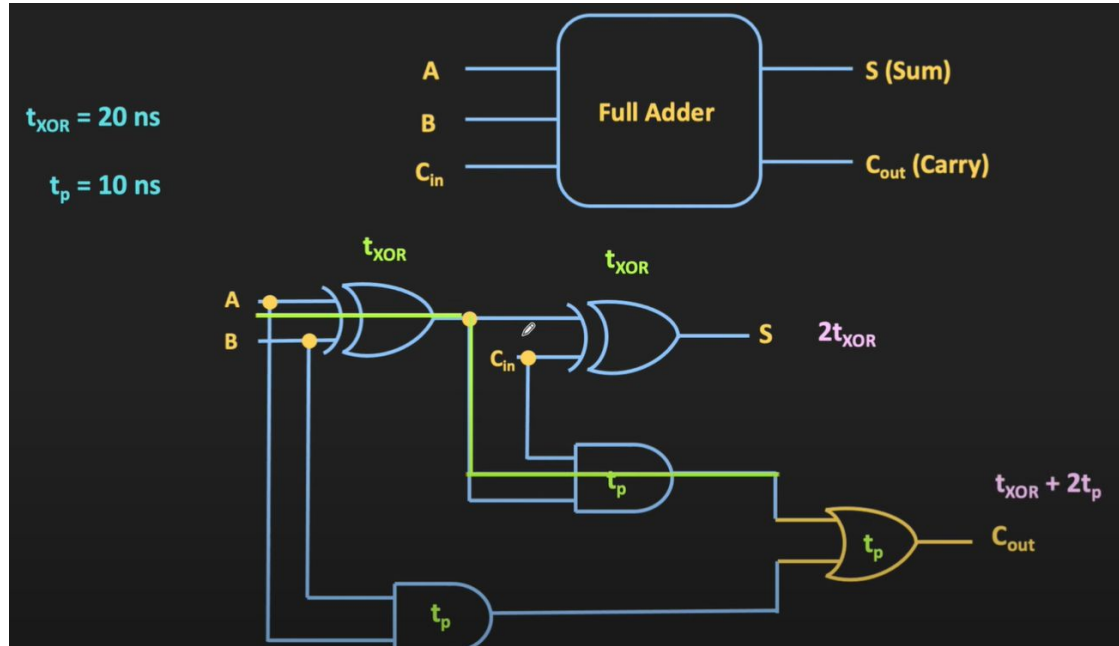
Prop delay of Ripple Carry Adder with gate delays (2)



Propagation delay for sum
given $T(xor)$ and $T(p)$ is
 $2T(xor)$

Propagation delay for Carry
given $T(xor)$ and $T(p)$ is
 $T(xor) + 2T(p)$

 Prop delay of Ripple Carry Adder with gate delays (3)




By applying the formula we derived earlier, the worst case delay for sum and carry is 160ns

But as we know the internal circuitry now and propagation delay of the logic gates, we can find the propagation delay of sum and carry even more accurately

$$\text{Carry Propagation Delay} = 4 \times 40 \text{ ns} = 160 \text{ ns}$$

$$\text{Valid Sum output} = (3 \times 40) + 40 = 160 \text{ ns}$$

 Prop delay of Ripple Carry Adder with gate delays(4)



Calculation of S_1 :

Delay for 1st XOR gate is $T(xor)$


For the second XOR gate, It needs C_1 as input and it takes $T(xor) + 2T(P)$

Hence total time taken for S_1 is $(2T(xor) + 2T(p))$

Calculation of C_1 :

$T(xor) + 4T(p)$

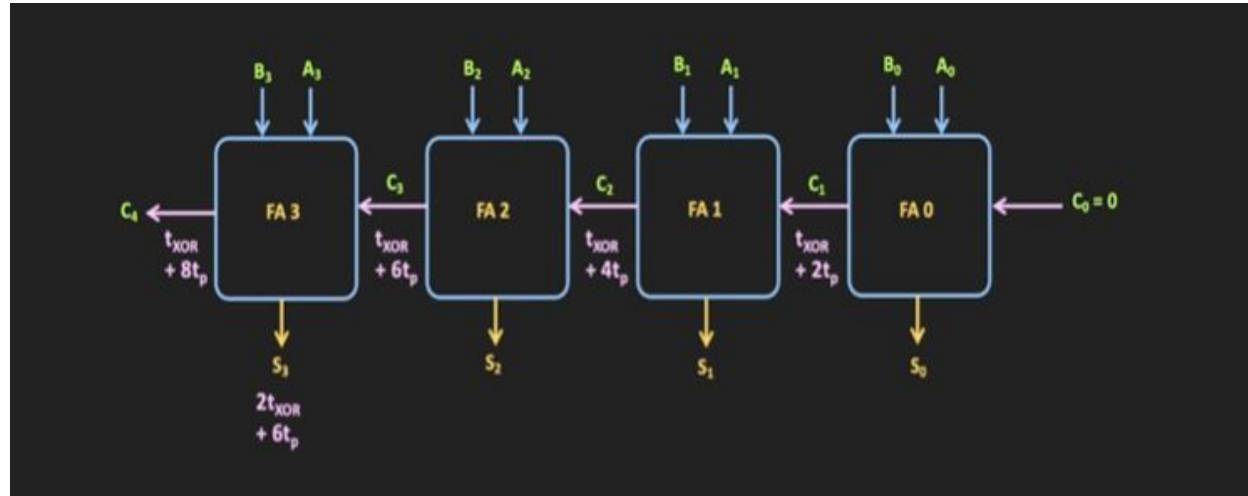Prop delay of Ripple Carry Adder with gate delays(4)



So, applying the same to all the Sums and Carry of
Ripple carry adder

$$S_3 = 2T(\text{XOR}) + 6T(\text{P})$$

$$C_4 = T(\text{xor}) + 8T(\text{P})$$

For n bit Ripple Carry adder

Stable Carry output C_{n+1} is available after $t_{\text{XOR}} + 2n t_p$

Stable Sum output S_n is available after $2t_{\text{XOR}} + 2(n-1)t_p$