
 



# HALF ADDER

 


```
module ha(A,B,Sum,Carry);  
input A,B;  
output Sum,Carry;  
assign Sum=A^B;  
assign Carry=A&B;  
endmodule
```




# FULL ADDER

 

```
module ha(A,B,C,Sum,Carry);  
input A,B,C;  
output Sum,Carry;  
assign Sum=A^B^C;  
assign Carry=(A&B)|(B&C)|(C&A);  
endmodule
```

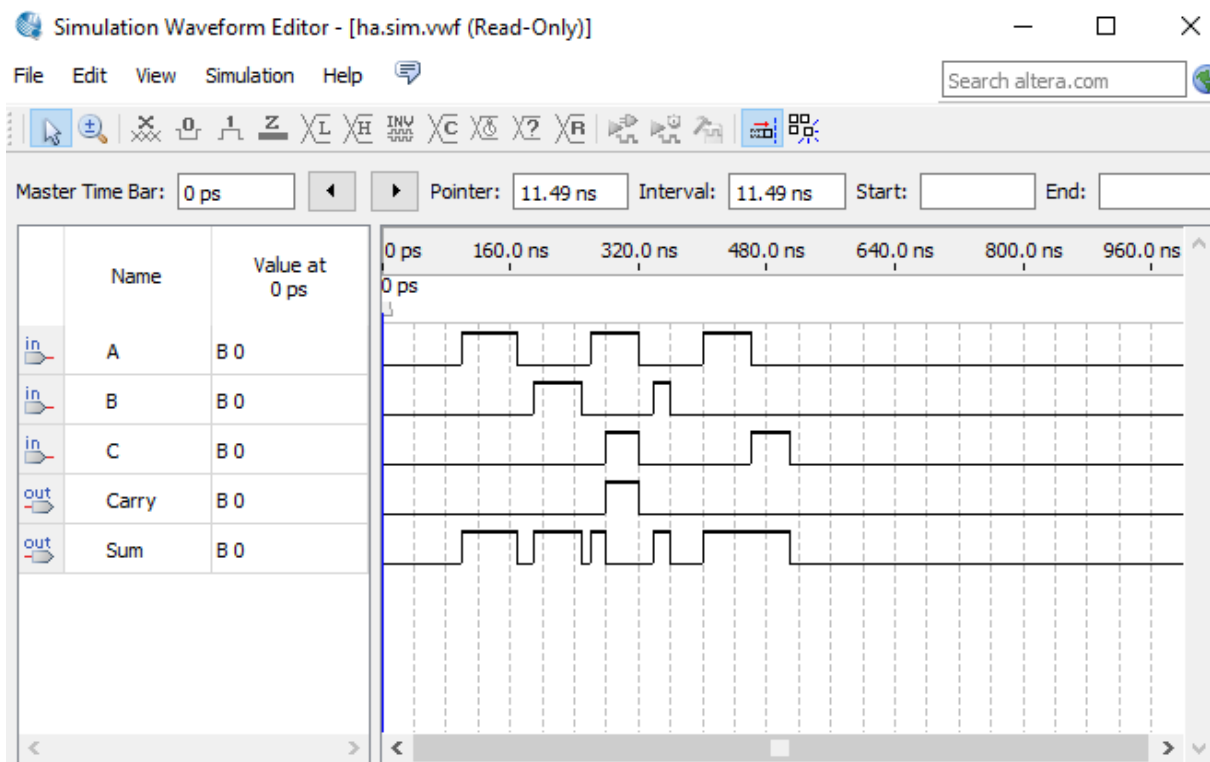


## HALF SUBTRACTOR

 


```

module ha(A,B,Difference,Borrow);
input A,B;
output Difference,Borrow;
assign Difference=A^B;
assign Borrow= ~A&B;
endmodule

```

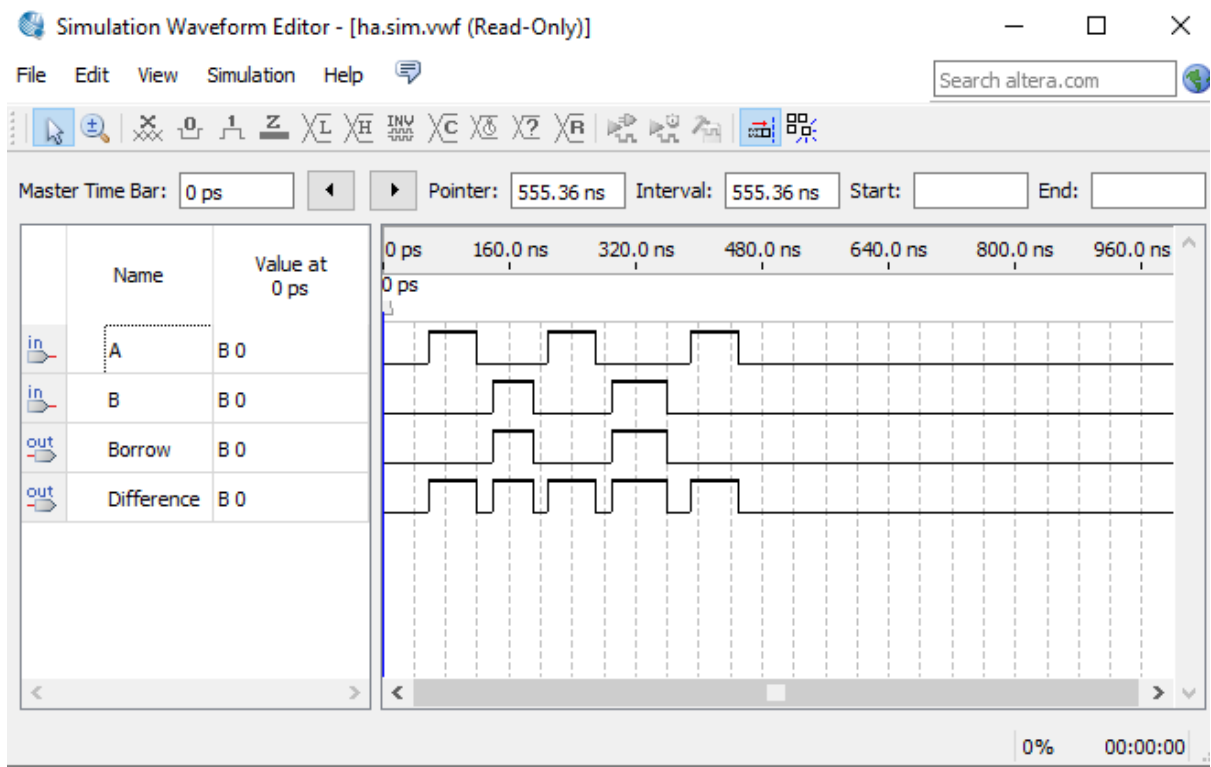

## FULL SUBTRACTOR

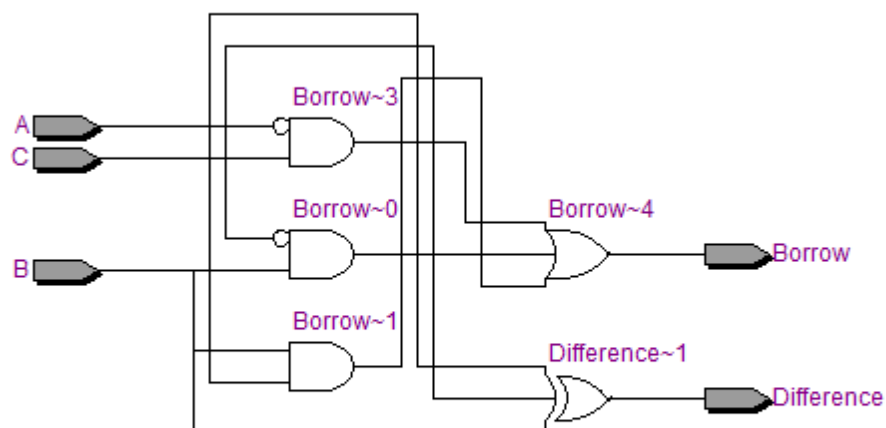


```
module ha(A,B,C,Difference,Borrow);
```


```

input A,B,C;
output Difference,Borrow;
assign Difference=A^B^C;
assign Borrow= (~A&B)|(B&C)|(C&~A);
endmodule

```

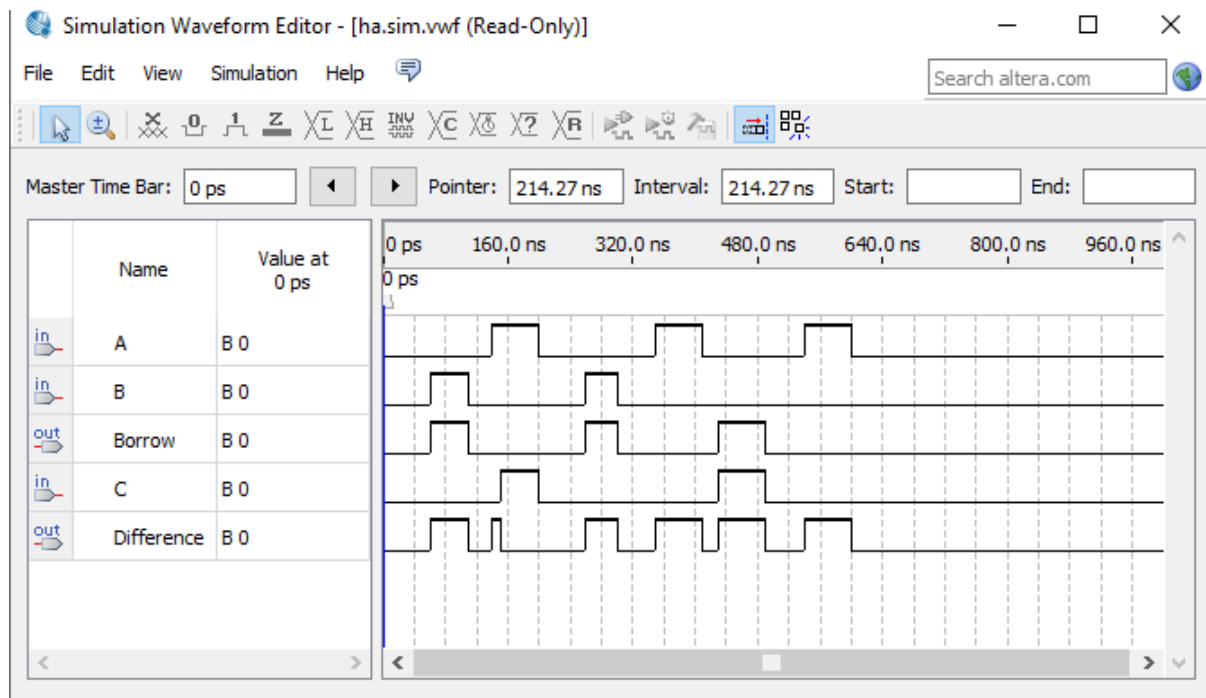


4:1 MULTIPLEXER

 


```

module m31(out,in0,in1,in2,in3,s0,s1);
output out;//output port
input in0,in1,in2,in3;//Input ports
input s0,s1;//Input ports:select lines
wire inv0,inv1;//Inverter Outputs
wire a0,a1,a2,a3;//AND gate outputs
not not_0(inv0,s0);
not not_1(inv1,s1);
and and_0(a0,in0,inv0,inv1);
and and_1(a1,in1,inv0,s1);
and and_2(a2,in2,s0,inv1);
and and_3(a3,in3,s0,s1);
or or_0(out,a0,a1,a2,a3);
endmodule

```

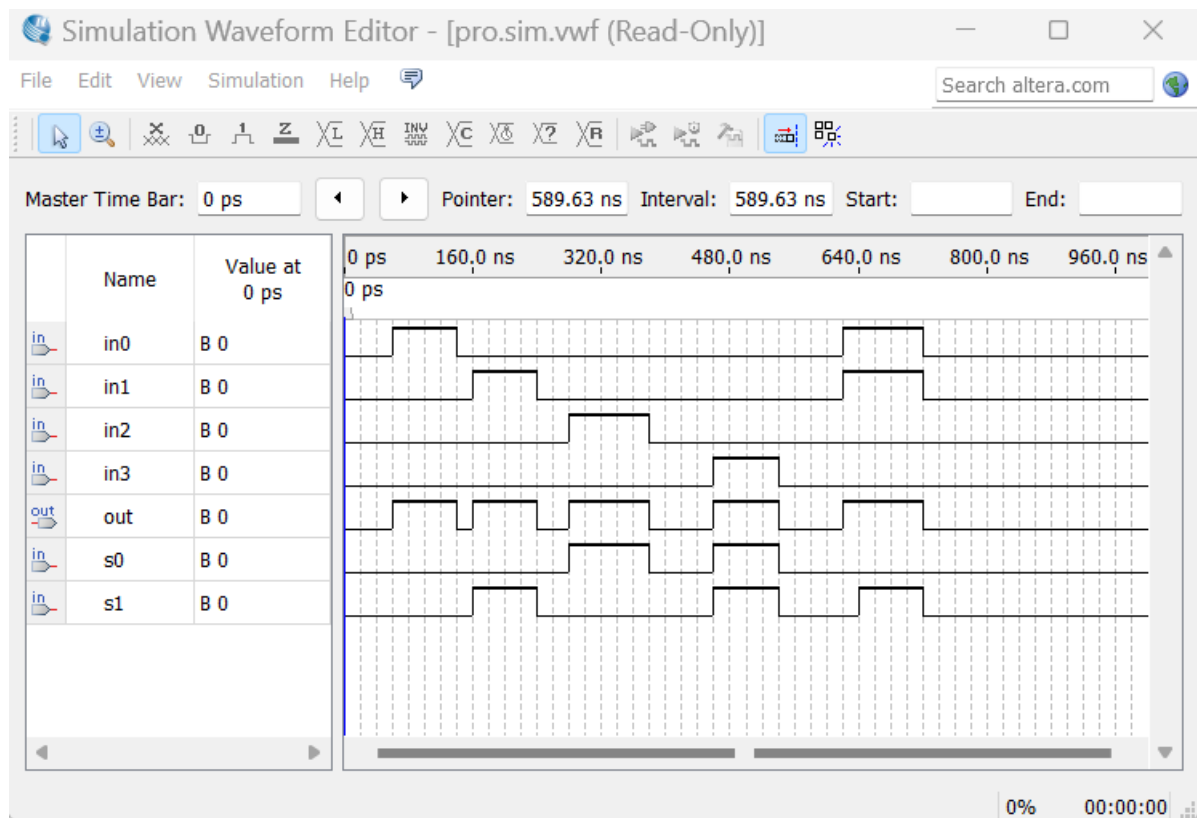

## DEMULTIPLEXER

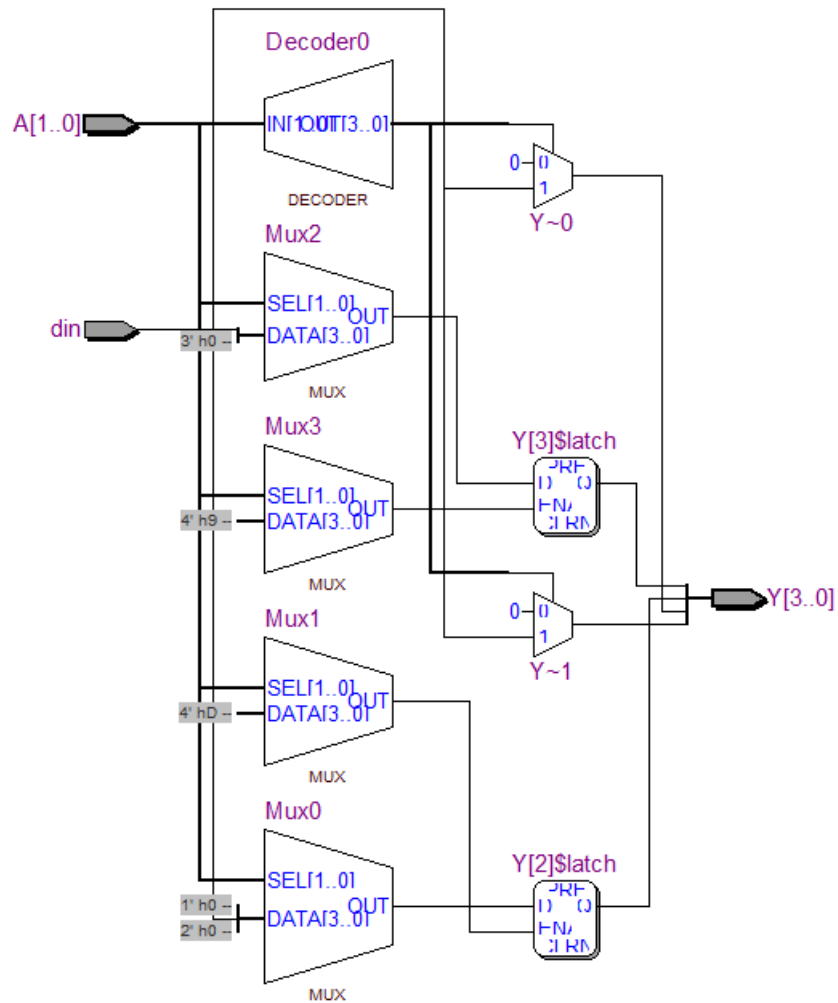


```

module pro (output reg [3:0] Y, input [1:0] A, input din);
always @(Y, A) begin
  case (A)
    2'b00 : begin Y[0] = din; Y[3:1] = 0; end
    2'b01 : begin Y[1] = din; Y[0] = 0; end
    2'b10 : begin Y[2] = din; Y[1:0] = 0; end
    2'b11 : begin Y[3] = din; Y[2:0] = 0; end
  endcase
end


```



endmodule

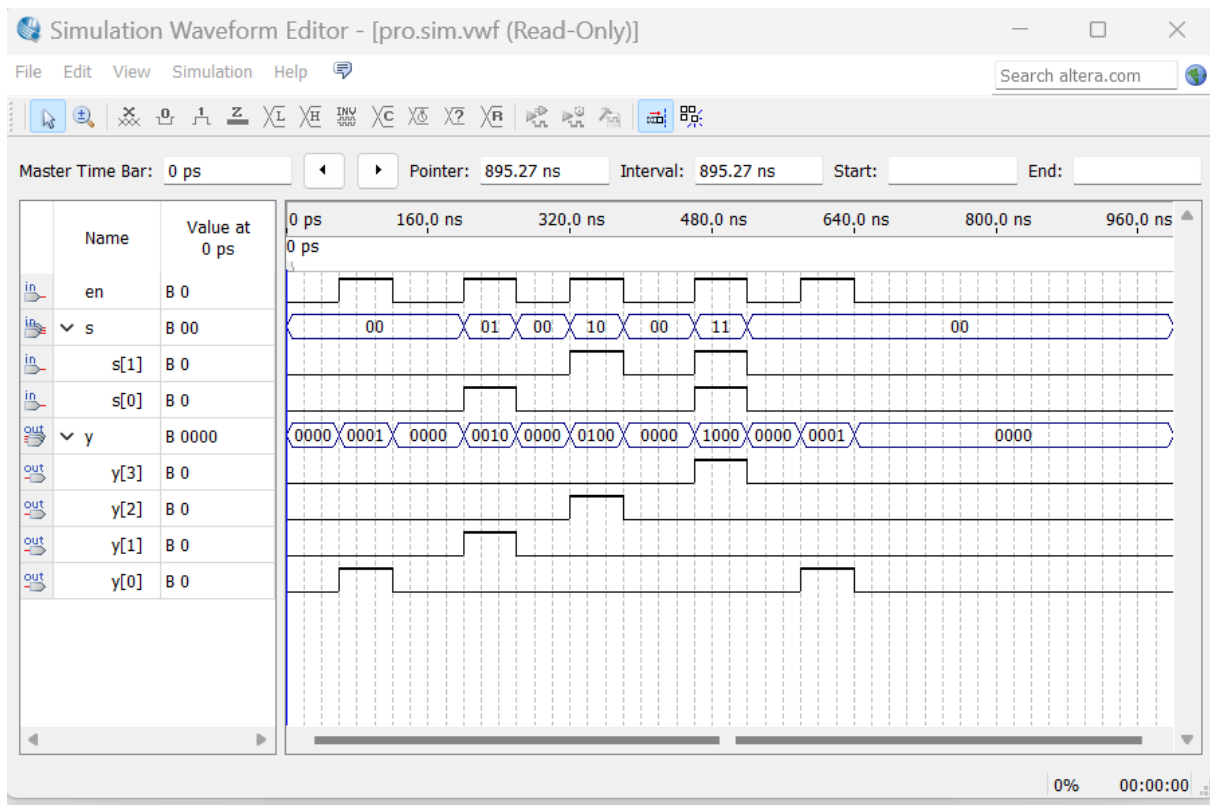

ENCODER

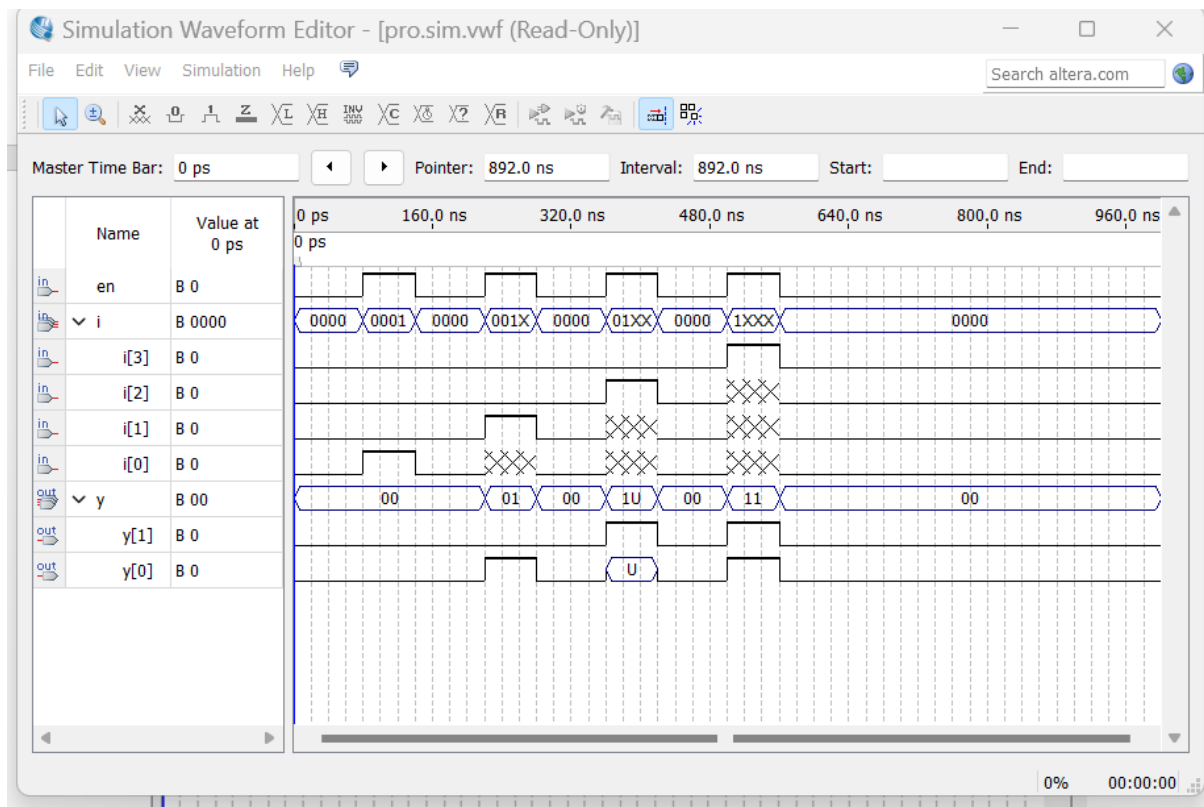

```
module priorityenc(en,i,y);
```

```
input en;
```


```
input [3:0]i;
```

```
output[1:0]y;
```


```
assign y[1]=i[2]||i[3]&en;
```

```
assign y[0]=i[1]||i[3]&en;
```

```
endmodule
```

 

## DECODER

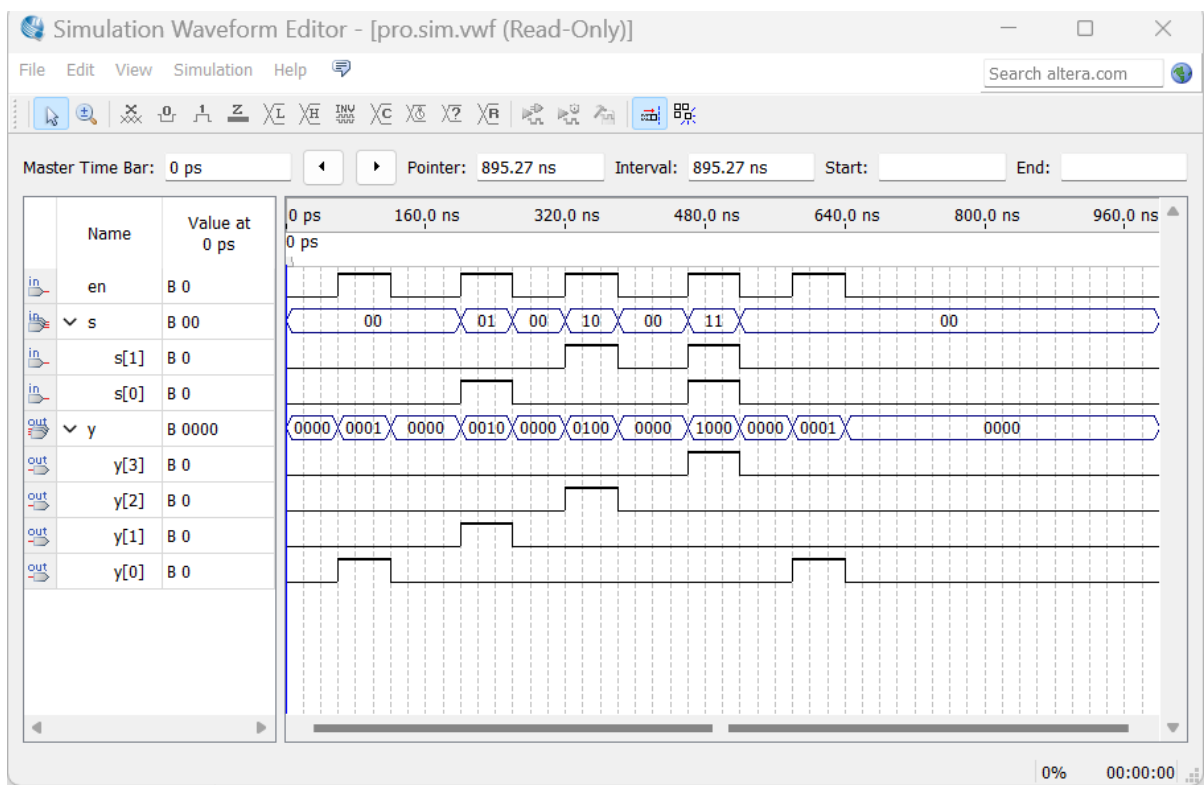

```
module decode(en,s,y);
```

```
input en;
```


```
input [1:0]s;
```

```
output[3:0]y;
```


```

assign y[0]=(~s[1])&(~s[0])&en;
assign y[1]=(~s[1])&(s[0])&en;
assign y[2]=(s[1])&(~s[0])&en;
assign y[3]=(s[1])&(s[0])&en;
endmodule

```

 


2 bit MAGNITUDE COMPARATOR

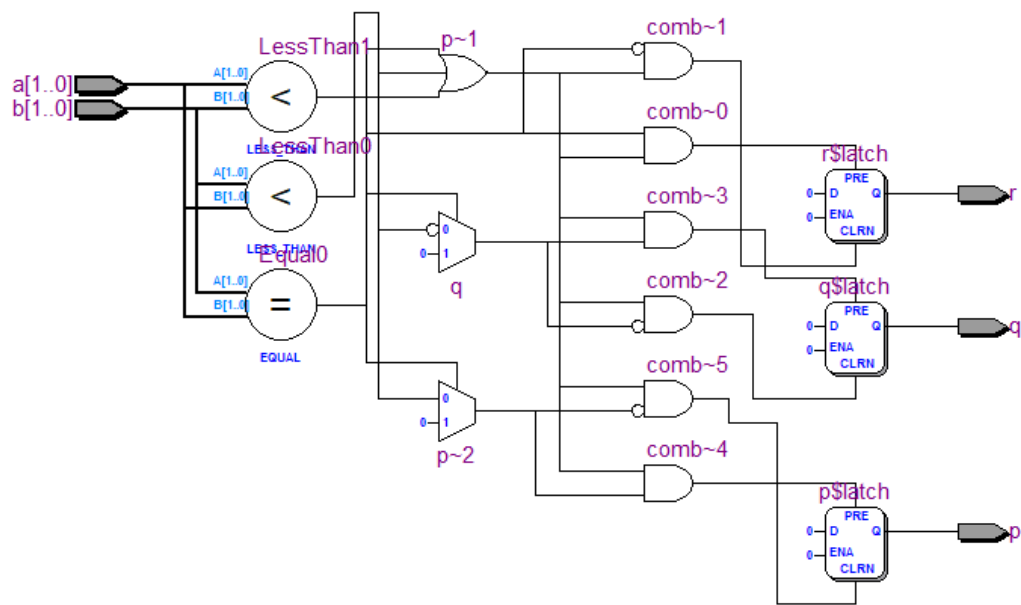

```

module pro(p,q,r,a,b);
input [1:0]a;
input [1:0]b;
output reg p,q,r;
always@(a or b)
begin
if(a==b) {p,q,r}=1'b001;
else if(a>b) {p,q,r}=3'b100;
else if(a<b) {p,q,r}=3'b010;
end
endmodule

```

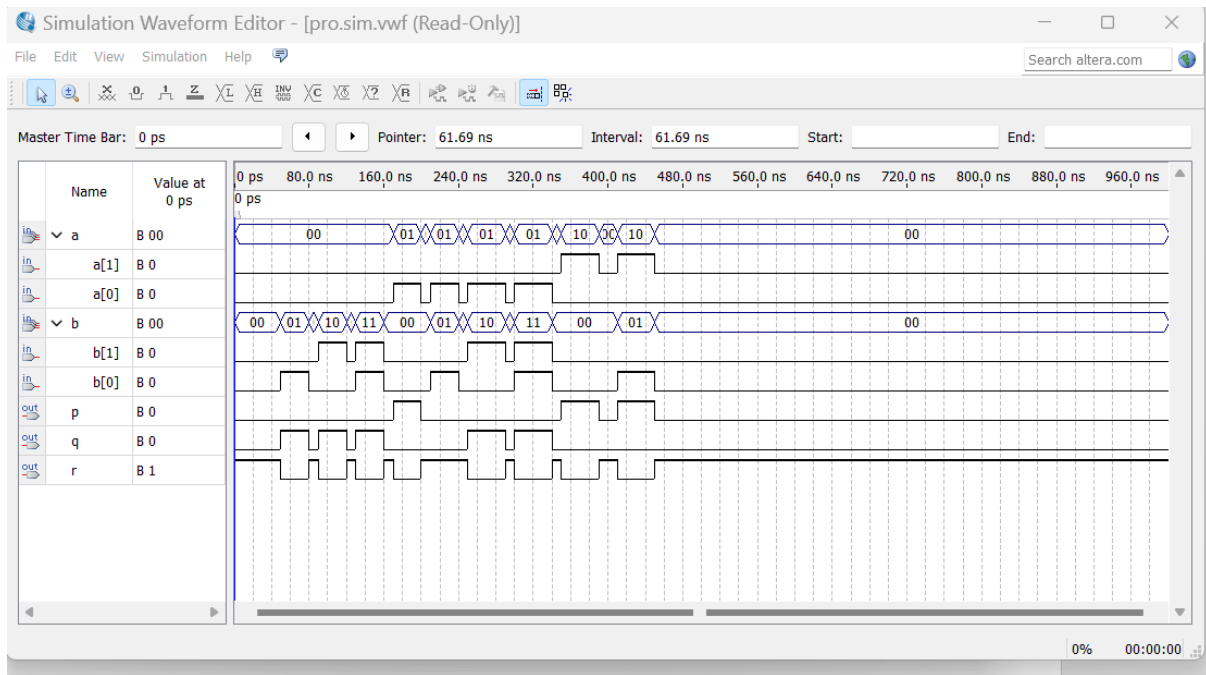

## SR FLIP FLOP

```
module pro(s,r,clk,clear,q,qbar);
```

```
input s,r,clk,clear;
```

```
output reg q,qbar;
```

```
always@(posedge clk)
```

```
begin
```

```
if(clear)
```

```
begin
```

```
q=0;
```


```
qbar=1;
```

```
end
```


```
else
```

```
begin
```
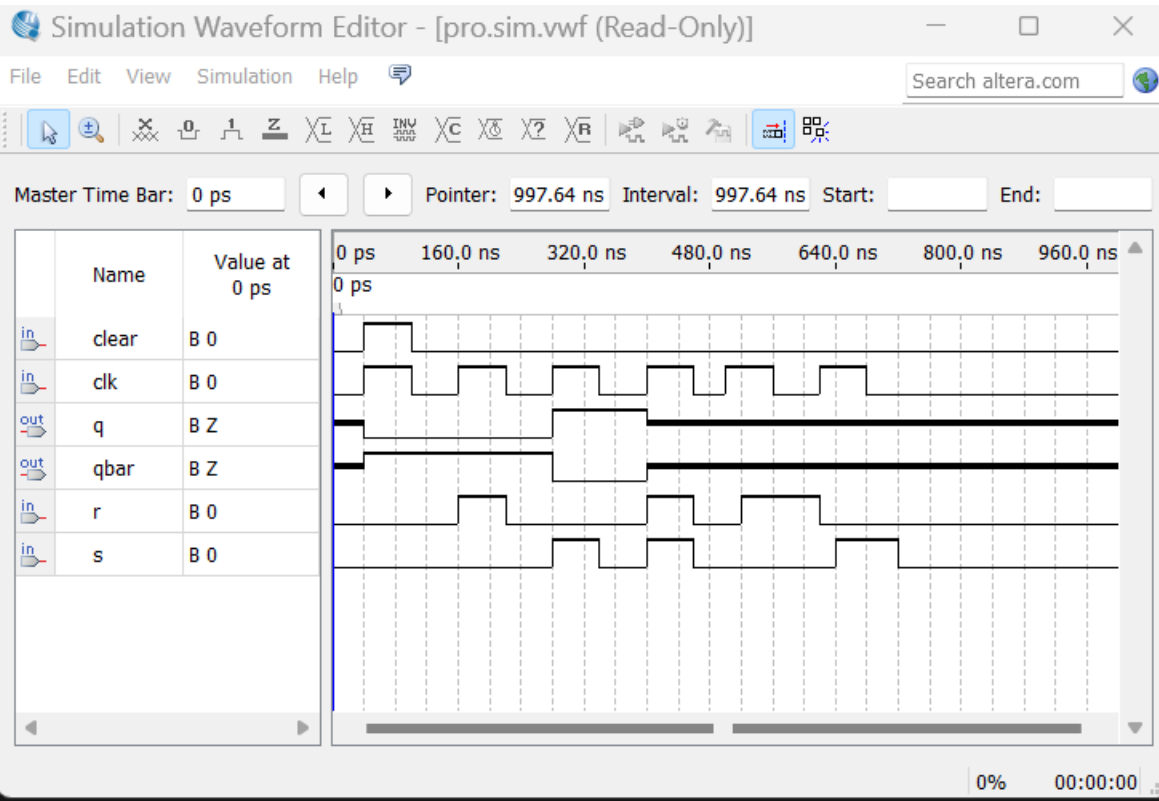
```
if(s!=r)
begin
q=s;
qbar=r;
end
else if(s==1&&r==1)
begin
q=1'bz;
qbar=1'bz;
end
end
end
endmodule
```





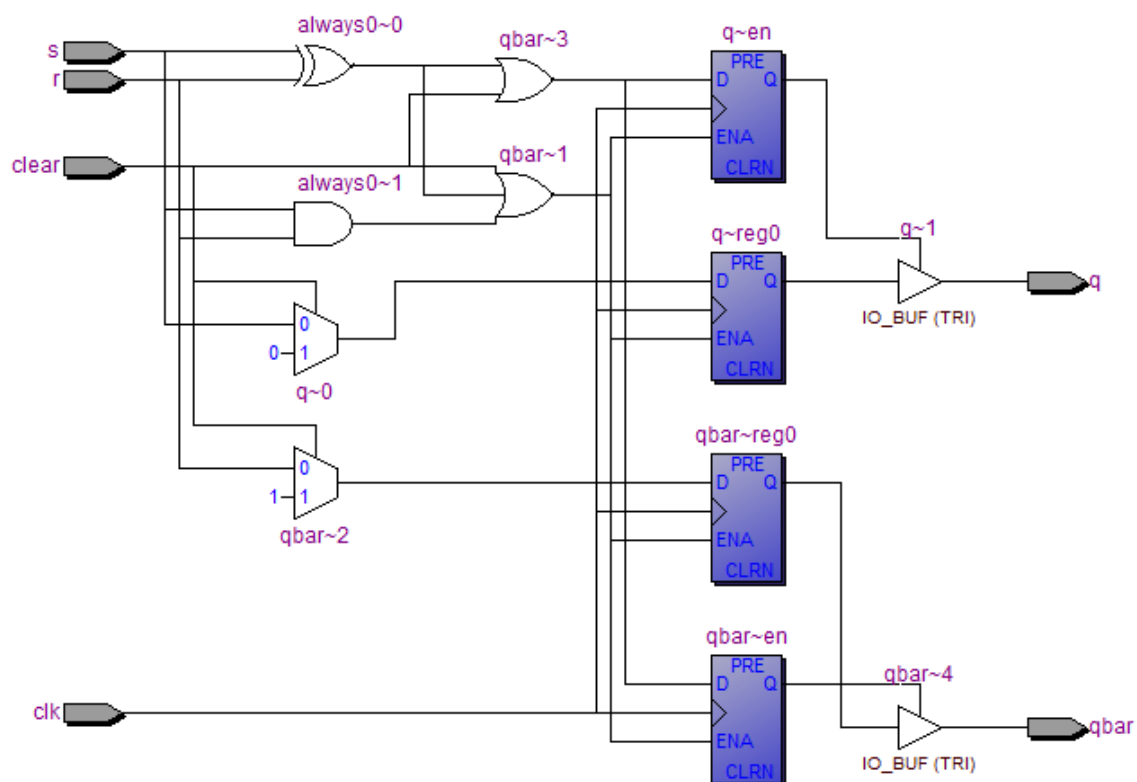

DFF

```
module pro(d,clk,clear,q,qbar);
```

```
input d,clk,clear;
```

```
output reg q,qbar;
```


```
always@(posedge clk)
```


```
begin
```

```
if(clear==1)
```


```
begin
```
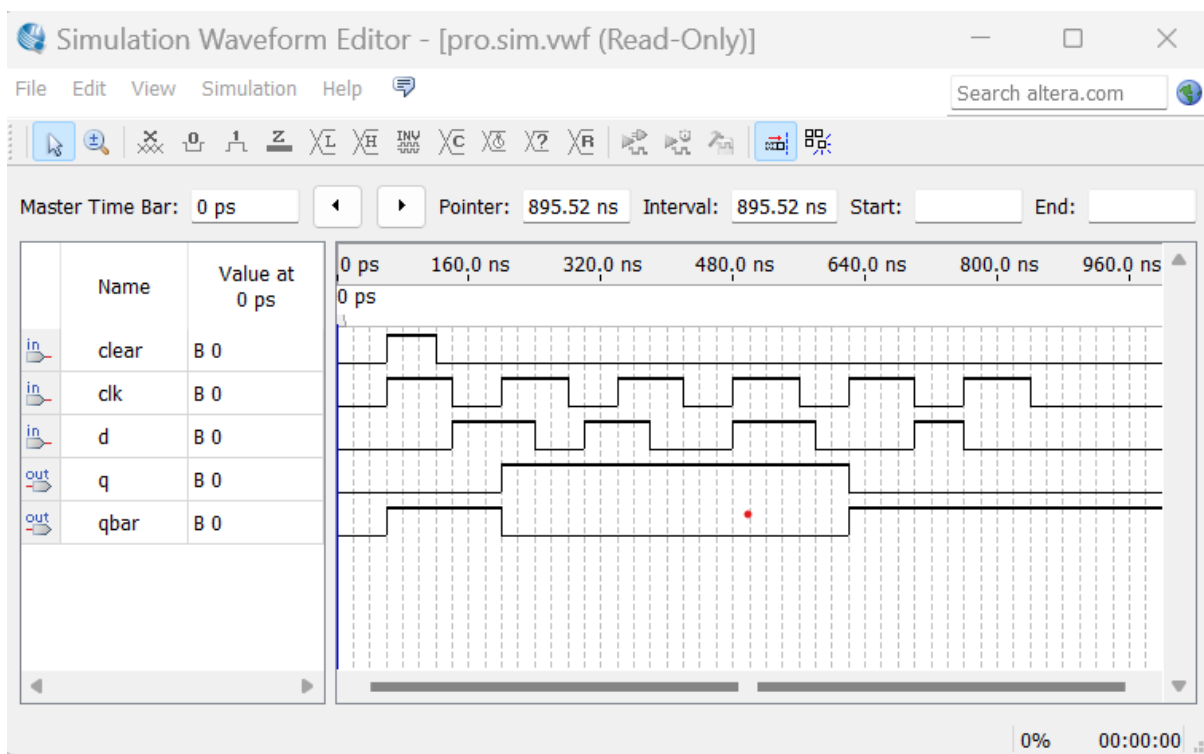
```
q=0;
qbar=1;
end
else
begin
q=d;
qbar=!d;
end
end
endmodule
```



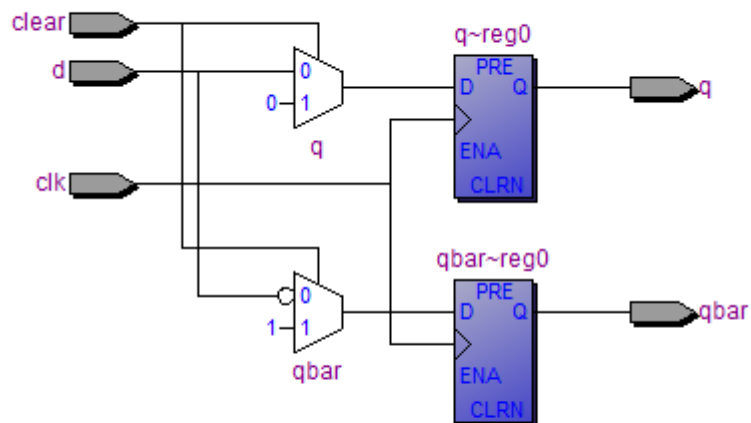

## JK FLIP FLOP

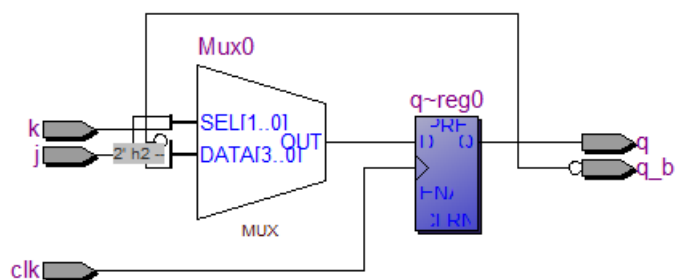

```


module pro(input j,k,clk,output reg
q,output q_b);
assign q_b=~q;
always @(posedge clk)

```

```

case ({j,k})
2'b00:q<=q;
2'b01:q<=1'b0;
2'b10:q<=1'b1;
2'b11:q<=!q;
endcase
endmodule

```

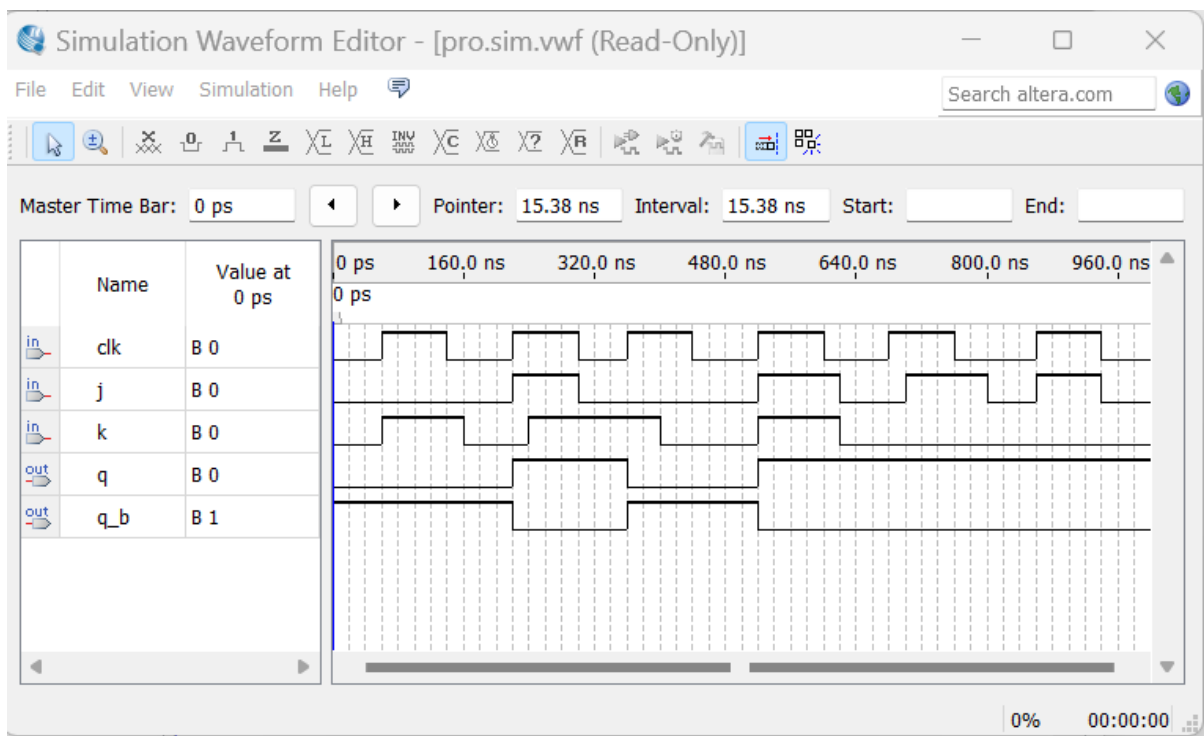



## SYNCHRONOUS COUNTER

```

module counter(clk,rst,count);
input clk,rst;
output reg[2:0]count;

```
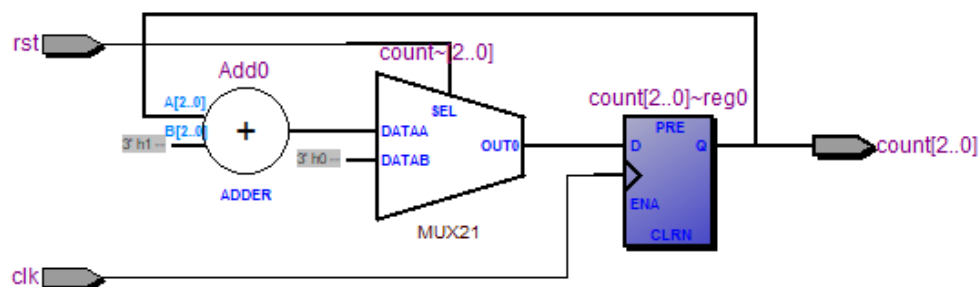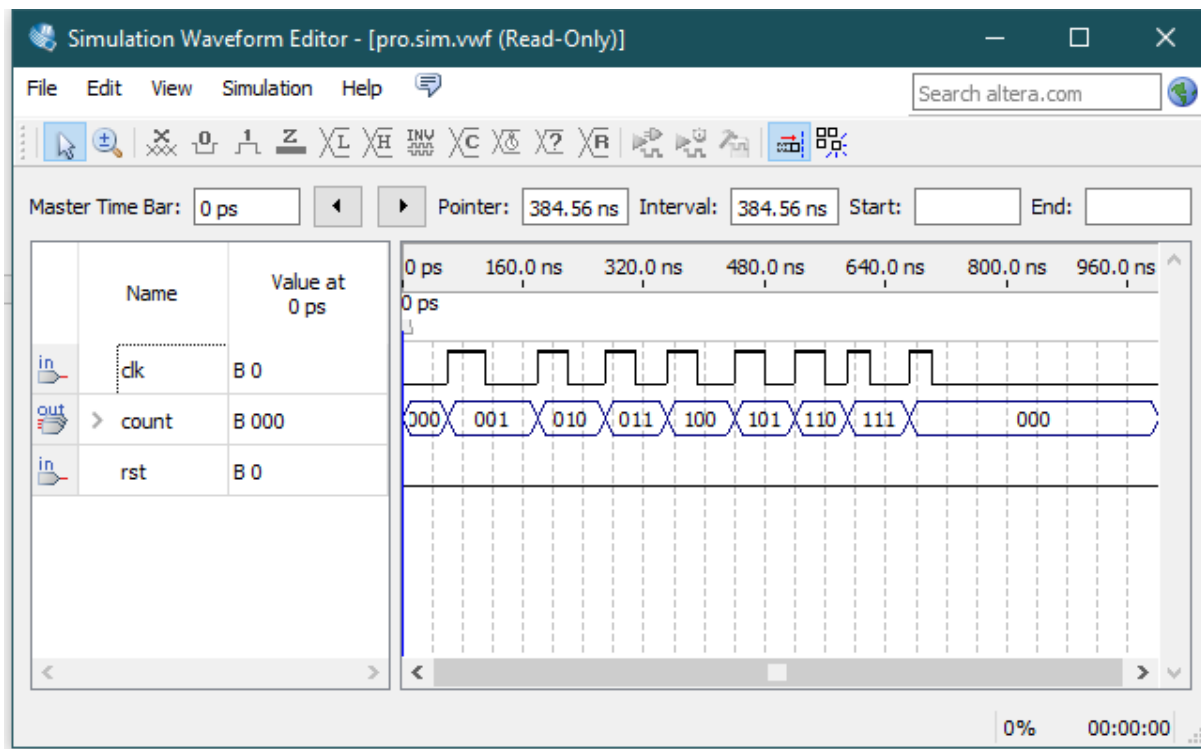
```
always @(posedge clk)
begin
if(rst==1)
begin
count=0;
end
else
begin
count=count+1;
end
end
endmodule
```





TFF

```
module pro(t,clk,clear,q,qbar);
```

```
input t,clk,clear;
```

```
output reg q,qbar;
```
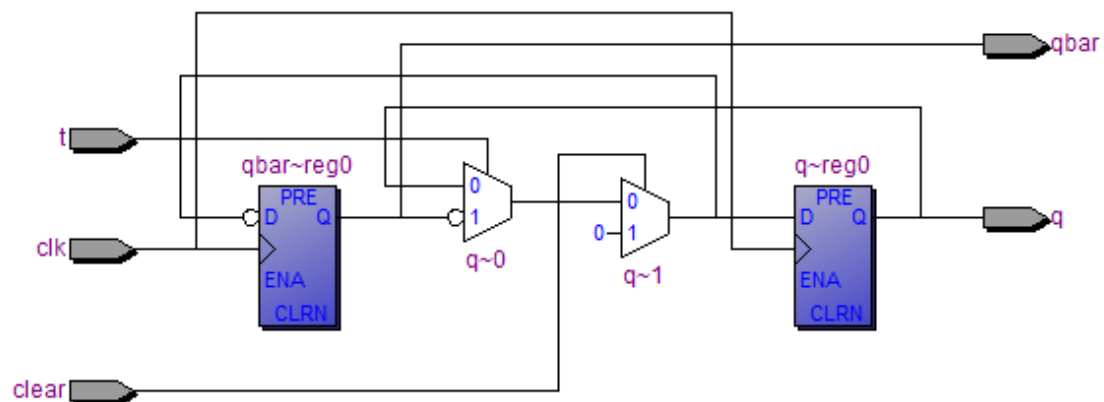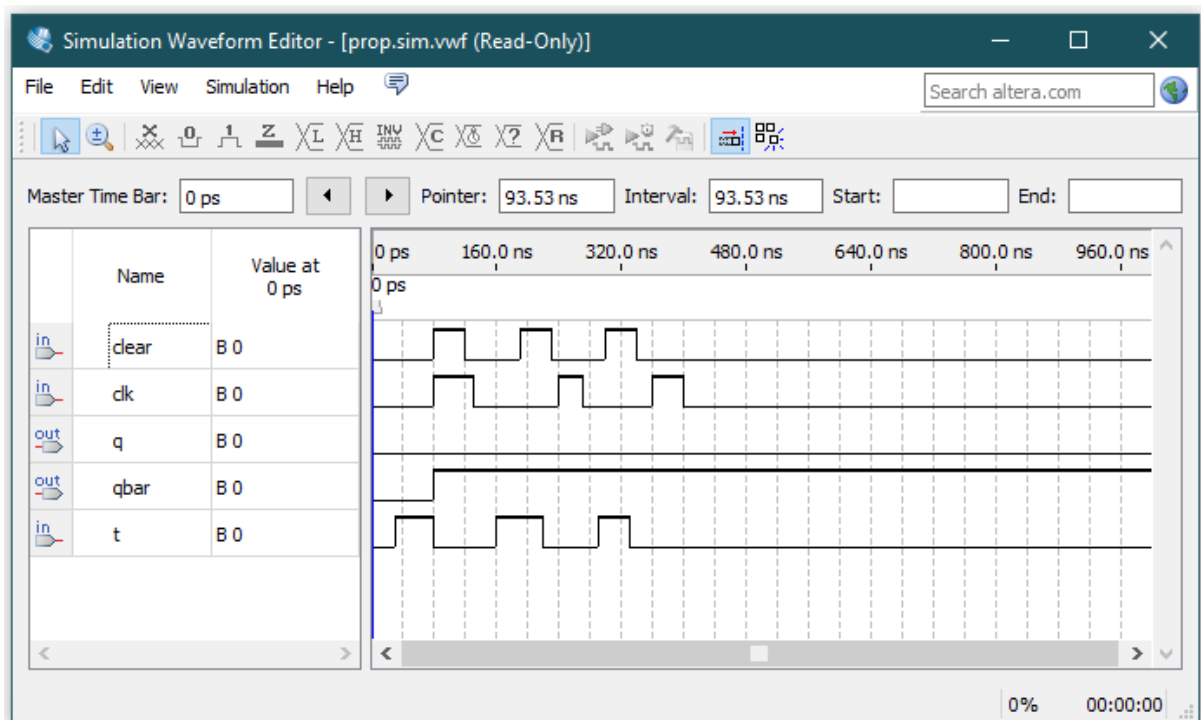
```
always@(posedge clk)
begin
if(clear==1)
begin
q=0;
qbar=1;
end
else if(t==1)
begin
q=~qbar;
end
else
begin
q=q;
end
qbar=~q;
end
endmodule
```





RIPPLE COUNTER

module expo(clk,count);


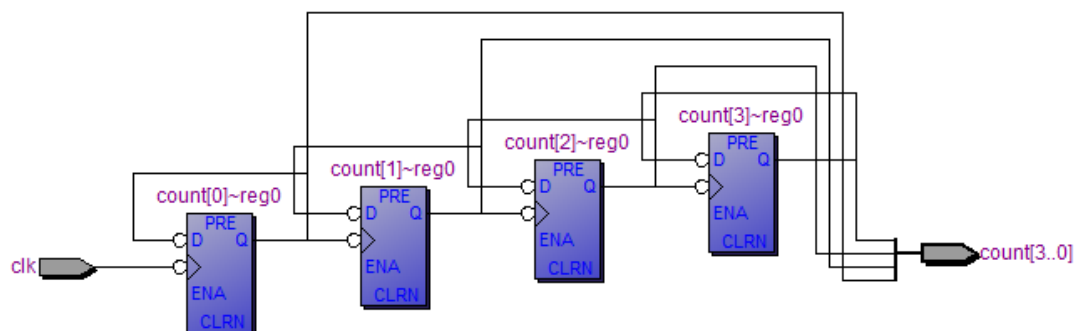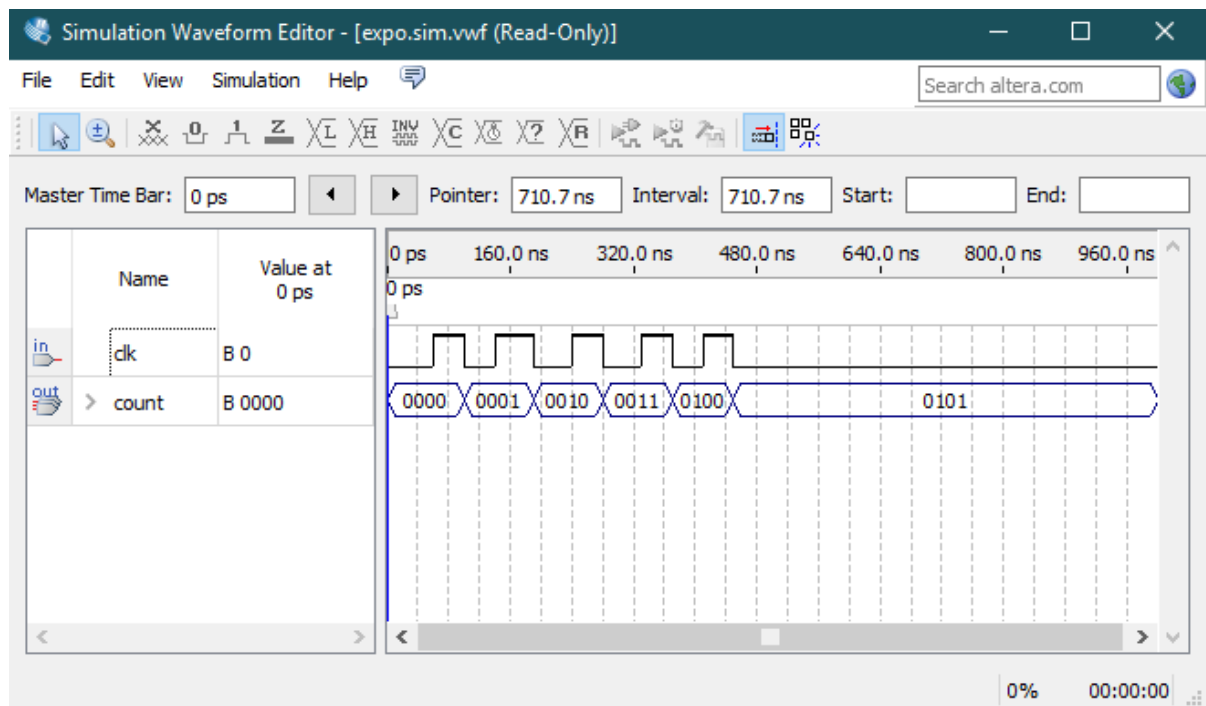
```
input clk;
output [3:0]count;
reg[3:0]count;
wire clk;
initial
count =4'b0000;
always@(negedge clk)
count[0]<=~count[0];
always@(negedge count[0])
count[1]<=~count[1];
always@(negedge count[1])
count[2]<=~count[2];
always@(negedge count[2])
count[3]<=~count[3];
endmodule
```





SISO Shift register

module expo (input clk,clear,si,output reg [3:0]so);

reg [3:0]tmp;
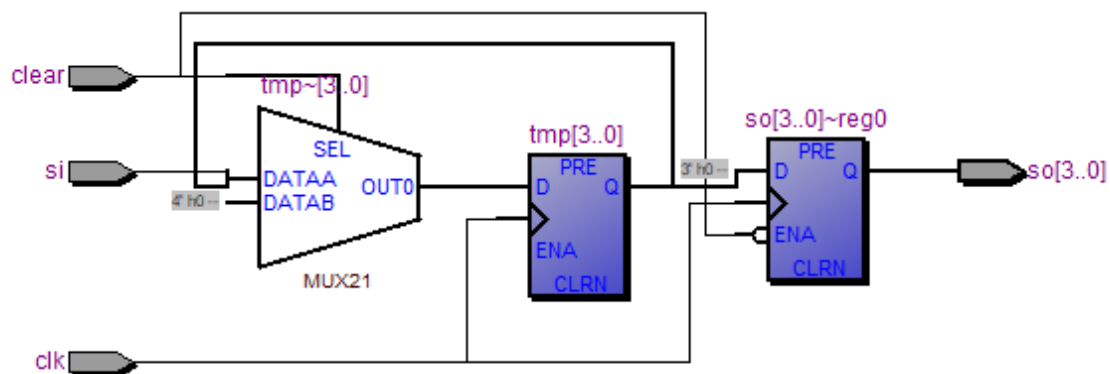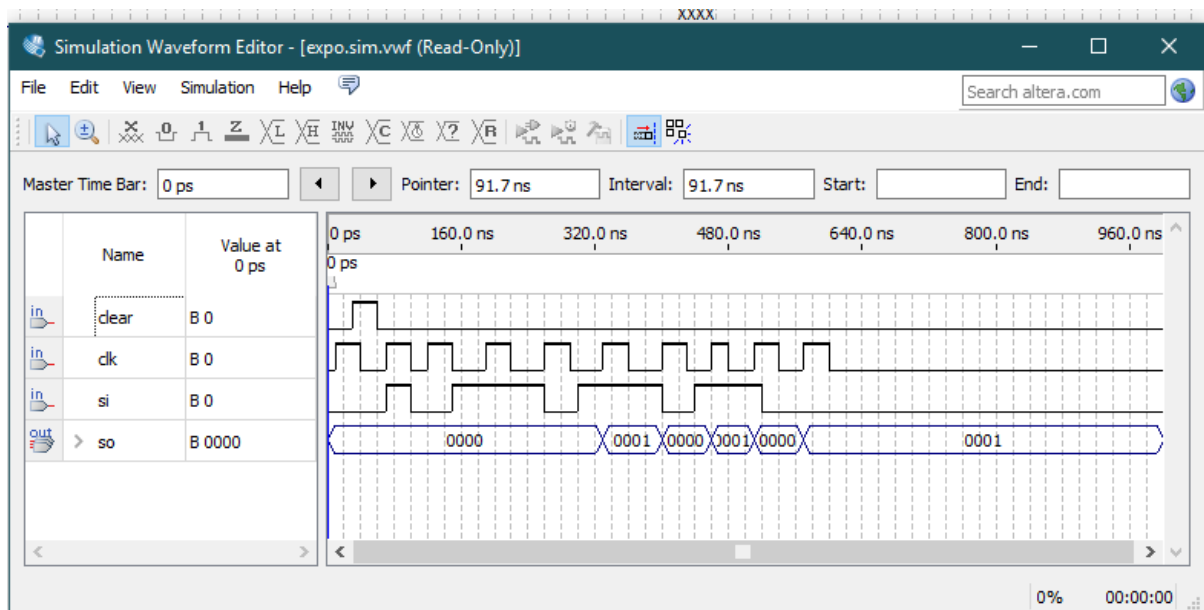
```
always @(posedge clk)
begin
if (clear)
begin
tmp<=4'b0000;
end
else
begin
tmp<=tmp<<1;
tmp[0]<=si;
so=tmp[3];
end
end
endmodule
```



SIPO

```
module propt(clk,clear,si,po);
```

```
input clk,si,clear;
```


```
output [3:0]po;
```


```
reg [3:0]tmp;
```

```

reg [3:0]po;
always @(posedge clk)
begin
if (clear)
tmp<=4'b0000;
else
tmp<=tmp<<1;
tmp[0]<=si;
po=tmp;
end
endmodule

```

 

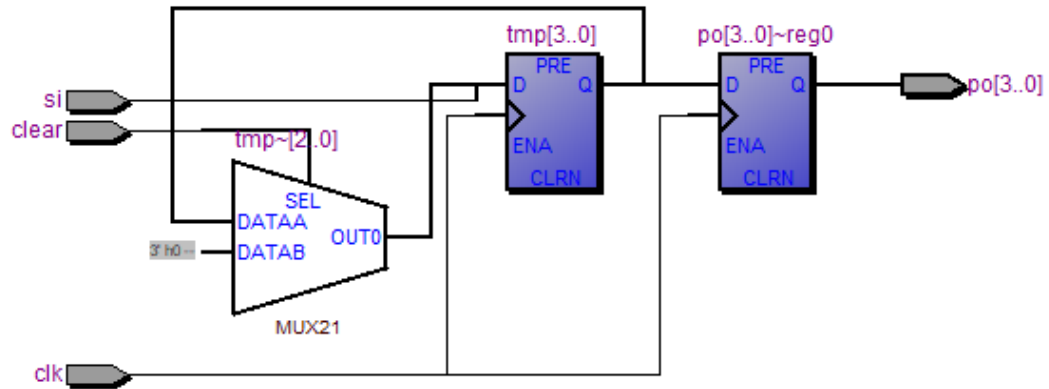

PIPO

```
module propy(clk,d,q);
```

```
input clk;
```

```
input [3:0]d;
```

```
output reg [3:0]q;
```

```
always @(posedge clk)
```

```
begin
```



```
q[3]=d[3];
```

```
q[2]=d[2];
```

```

q[1]=d[1];
q[0]=d[0];
end
endmodule

```

 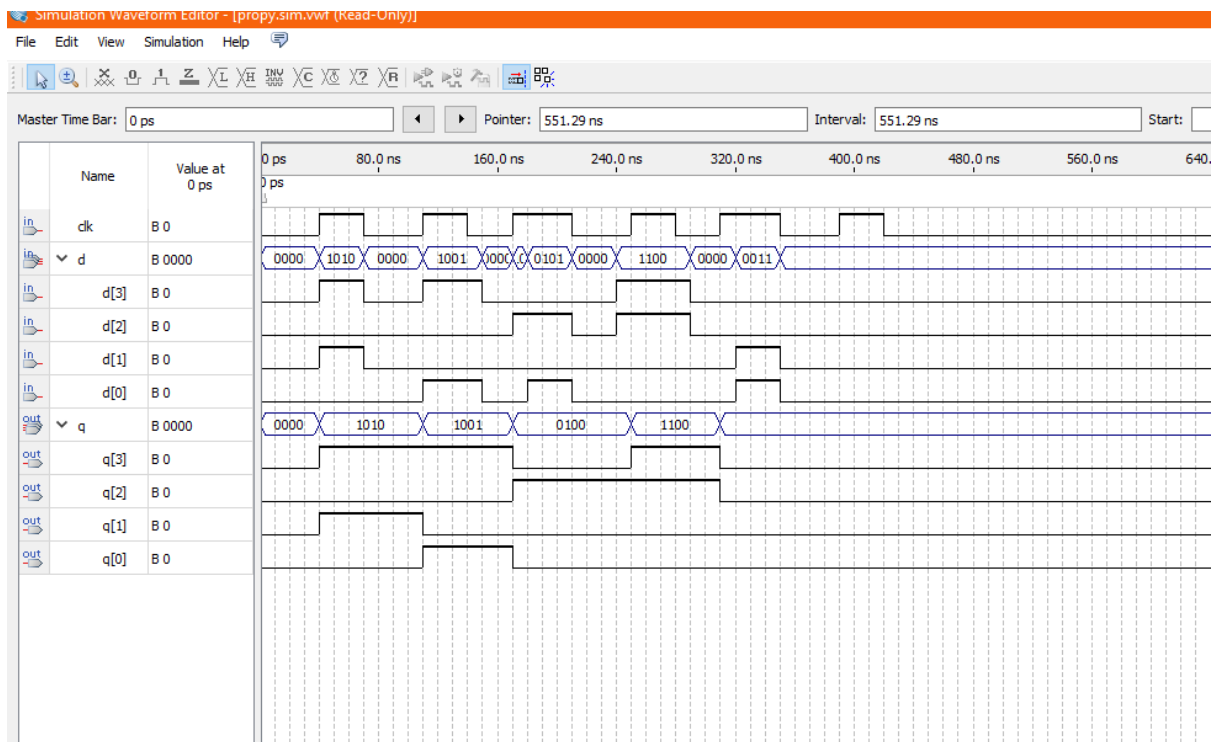

SEQUENCE DETECTOR

